

Matthew Loden

UIN: 808007439

Lab 1: Design of a Common-Emitter BJT Amplifier


Purpose:

The purpose of this lab was to use a single BJT amplifier to produce a given gain and within a level of swing and THD.

Calculations:


Included at End of Document

Schematics:

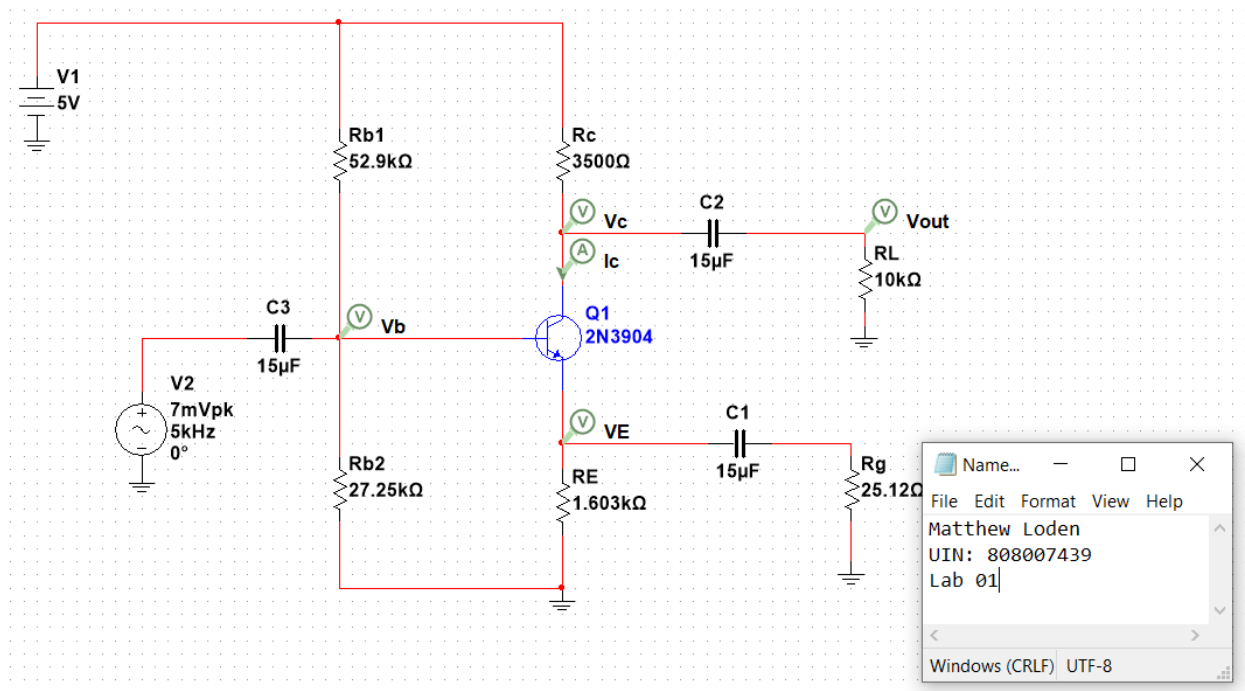


Simulations:


DC Operation Point

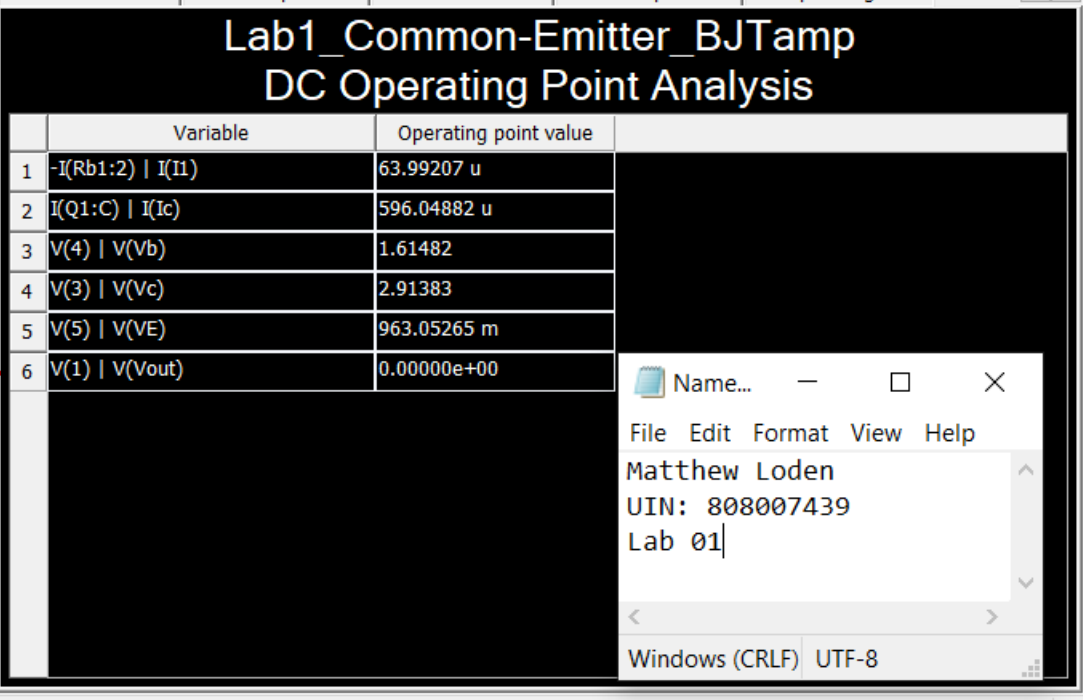


Magnitude of the Gain

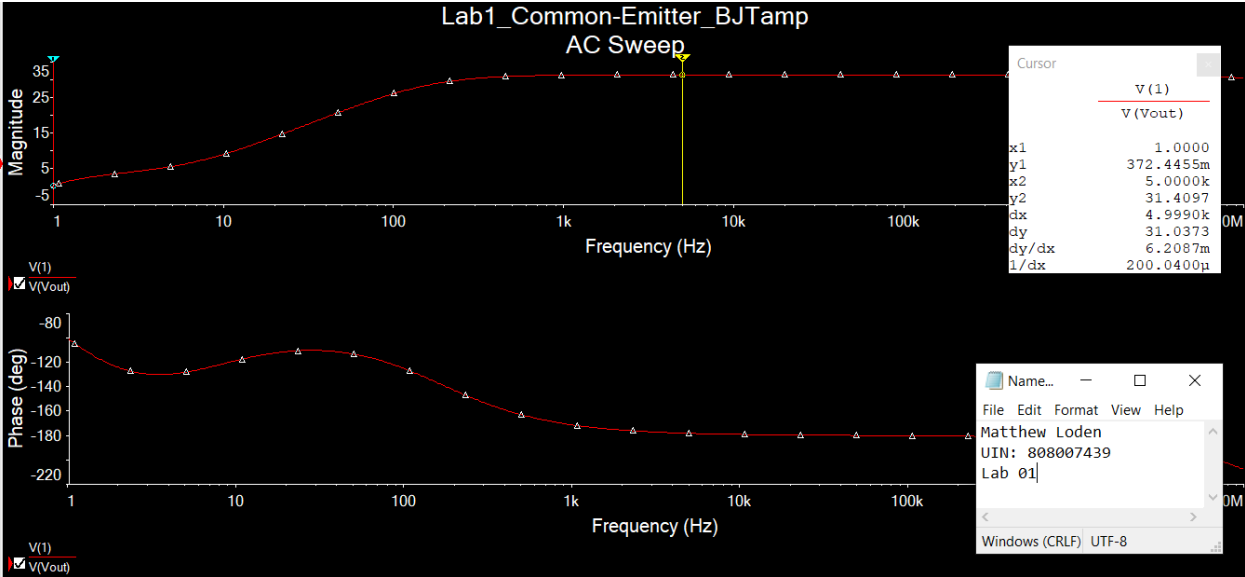


Waveform

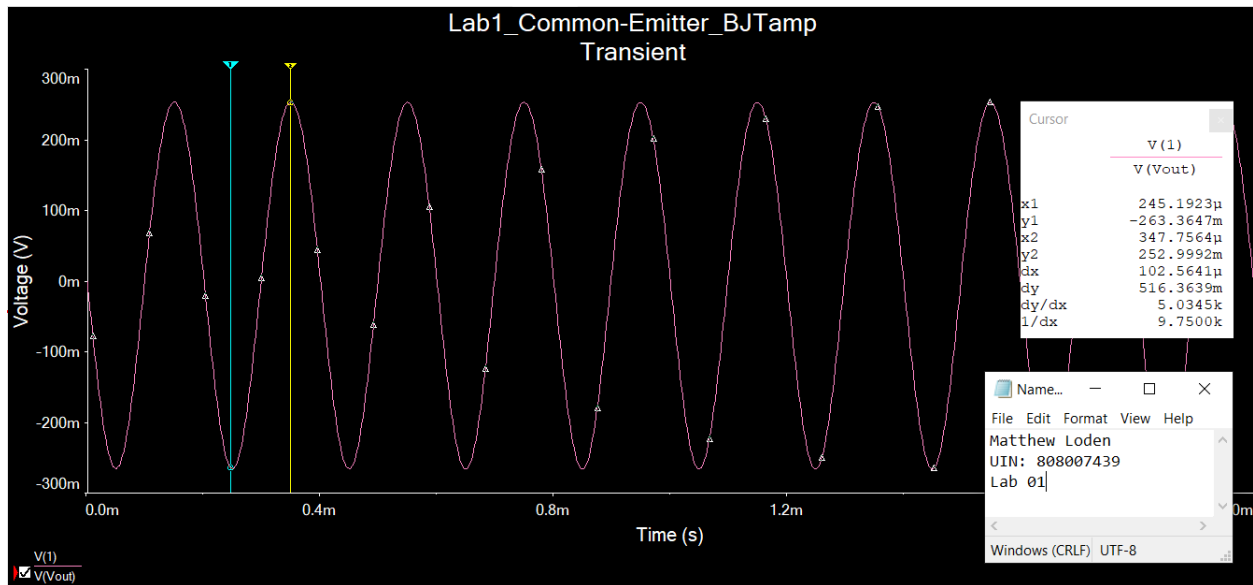


R in

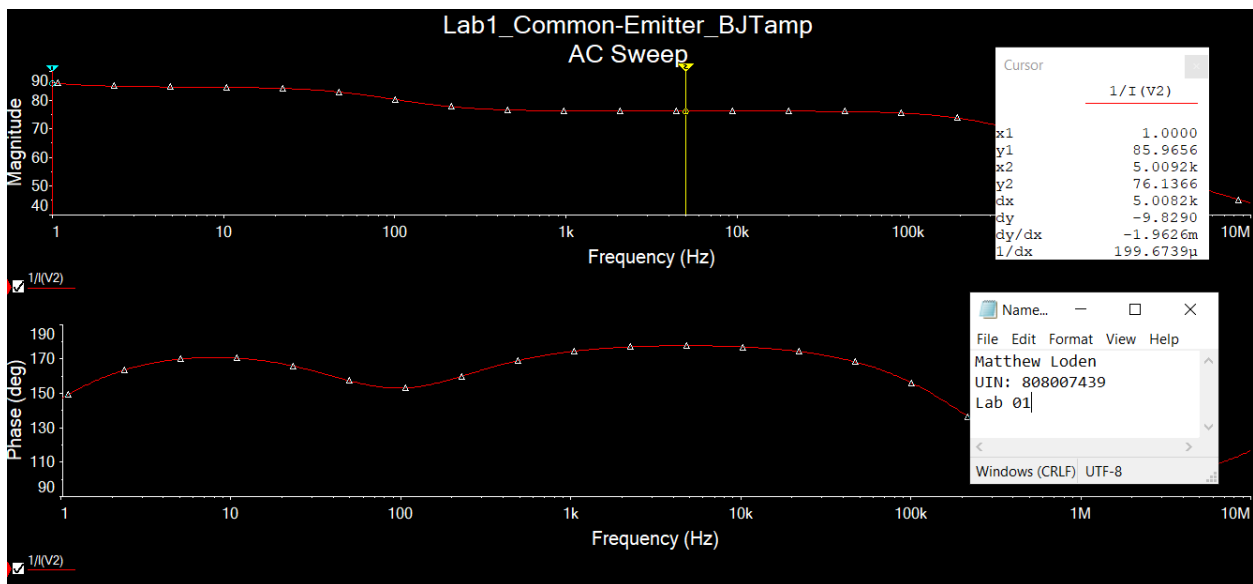

R out

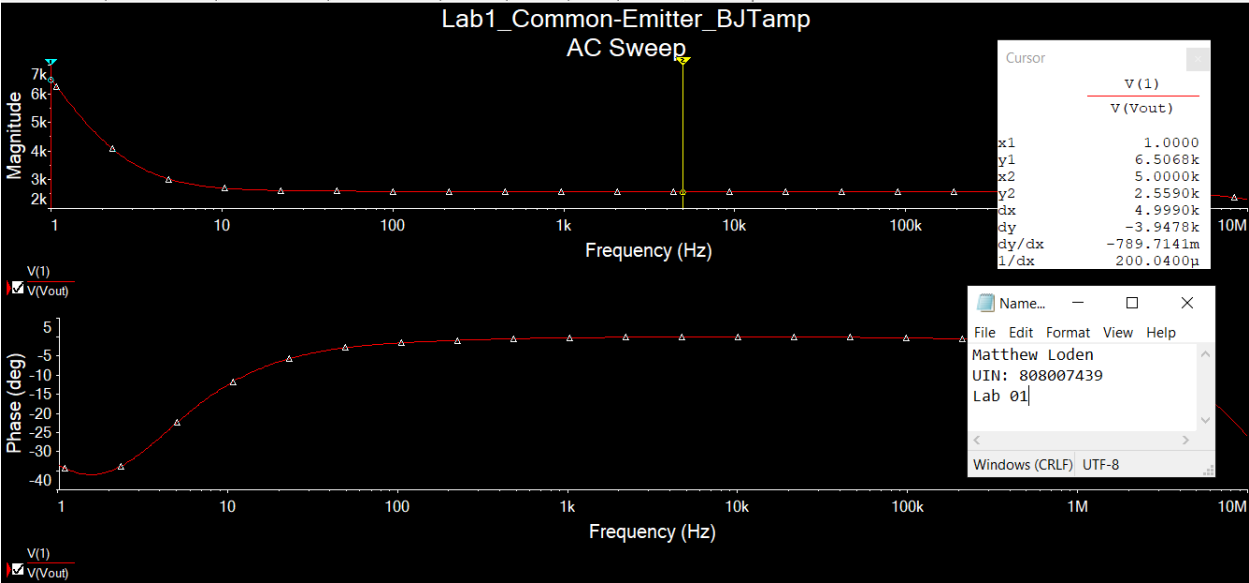


Fourier Simulation(THD)

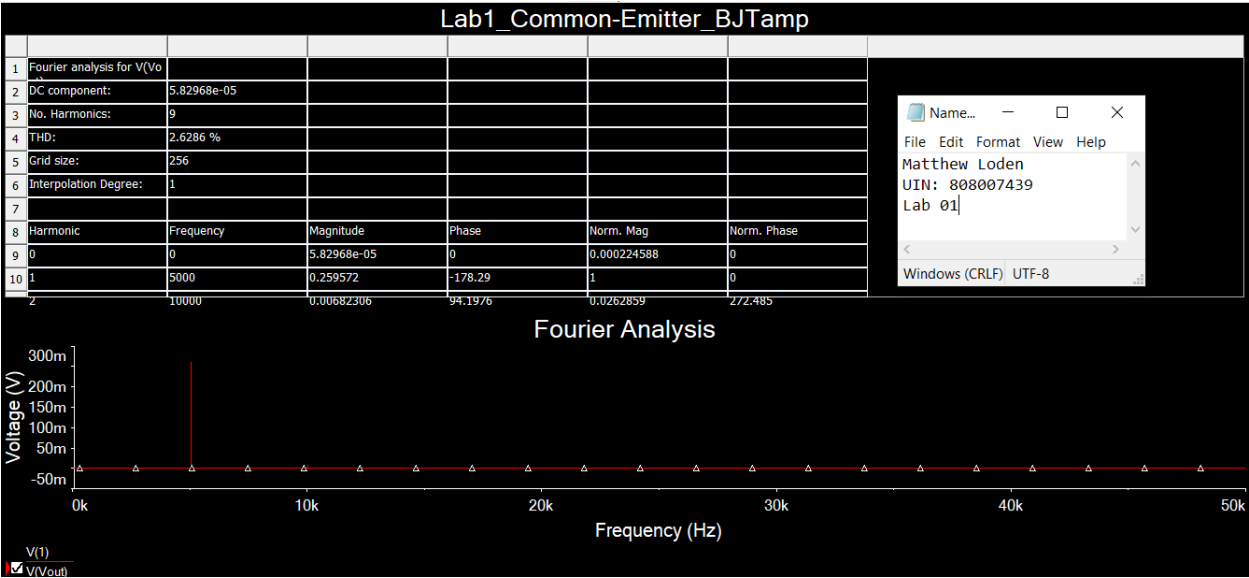


Measured


General Collected Data

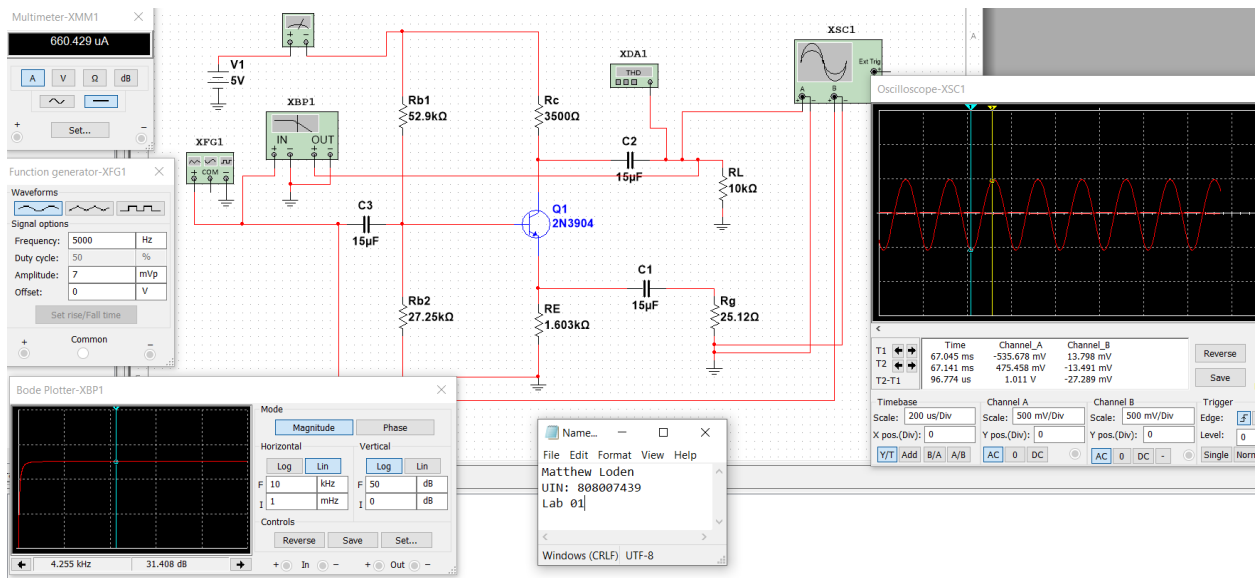

R in

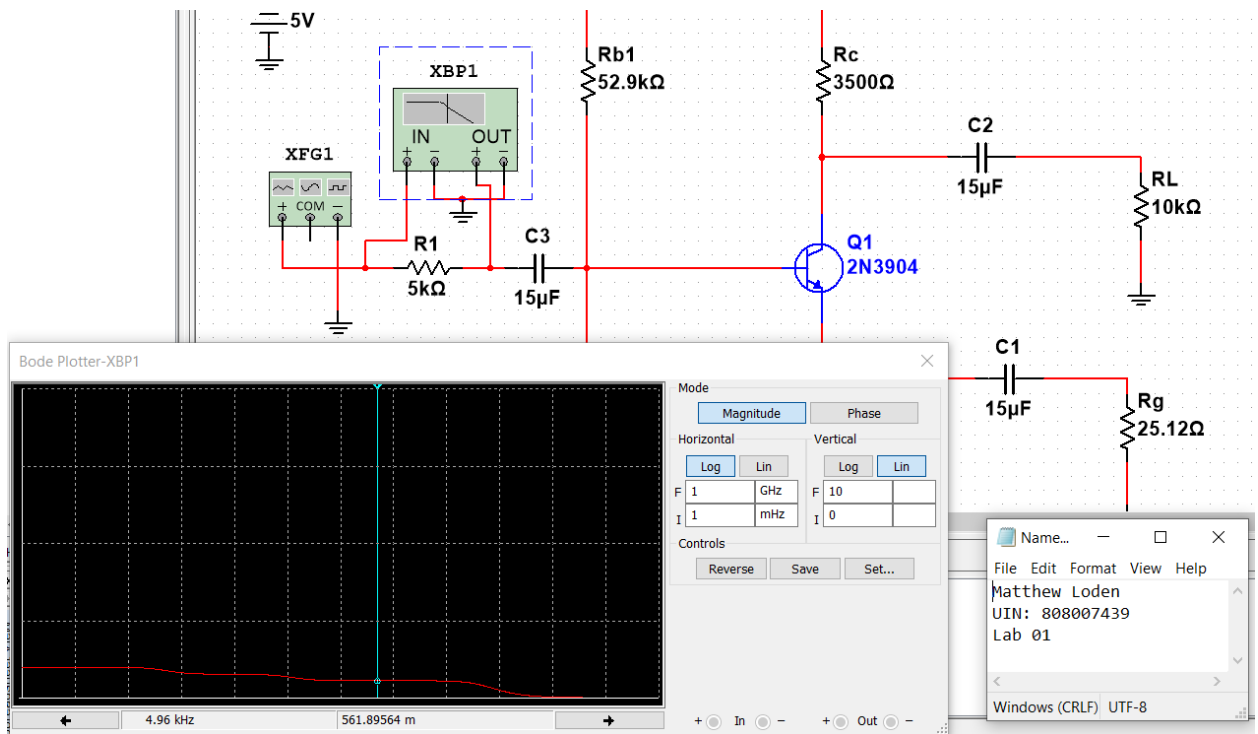


R out

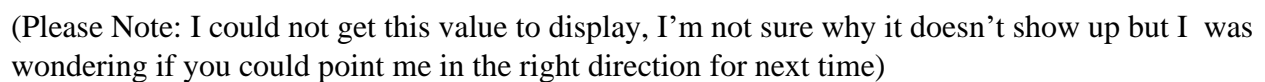

Value	Calculated	Simulated	Measured
V Emitter	1v	0.963v	0.964v
V Collector	2.1805	2.91383v	1.192v
V Base	1.7v	1.61482v	1.615v
Ic	0.6mA	0.596mA	1.49mA
Isupply	0.6623mA	0.6604mA	0.660429mA
Rin	5k Ω	5.0092k Ω	6.412k Ω
Rout	n/a	2.559k Ω	n/a

The measured and simulated results largely line up with the calculated values. Some discrepancies are in the voltage at the collector, the measured R_{in} and the R_{out} values. The voltage measured at the collector was very different based on the way the data was collected because I believe that there were errors on where I placed the probe for this point as the math is sound given that the current through the collector is the same for each data retrieval method. The R_{in} value is slightly off due to the transition from the math to the measurement simulation and then back to math. This flip-flopping of data retrieval caused the slight error. The last problem is the calculated value and measured value for R_{out} . I was not able to calculate the value of R_{out} directly by hand and my simulation for this measurement also failed. I'm not sure why either weren't successful, but I would like some pointers for future labs.

Lab 1

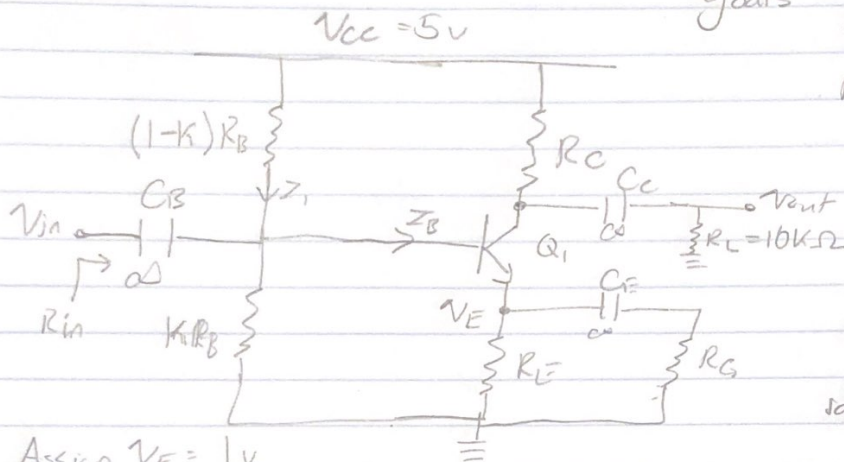

goals $V_E \geq 1V$ $R_{in} \geq 5k\Omega$
 $V_{CC} = 5V$ $|A_v| = 40$
 $R_L = 10k\Omega$ $I_S \leq 1.5mA$

$\beta = 190$

$$ratio = \frac{R_i}{R_i + 10k}$$

$R_{out} = 2.559k\Omega$
 calc

Assign $V_E = 1V$

$$V_X = V_{CC} - V_{CE,sat} - V_E = 5V - 0.2V - 1V = 3.8V$$

$$K = \frac{V_E + 0.7}{V_{CC}} = \frac{1.7}{5} = 0.34 \quad N = 10$$

$$Q = \frac{N V_X}{K(1-K)V_{CC}} = 33.86$$

$$R_C^2 (\beta R_L - R_{in,d} A_v) + R_C (2\beta R_L - 3R_{in,d} A_v - Q R_{in,d}) R_L - R_L^2 R_{in,d} (Q + 1) \geq 0$$

$$R_C^2 (17e^5) + R_C (2353300) 10k - 1.2467e^{14} \geq 0$$

$$R_C \geq 1.713k\Omega$$

$$R_C \leq R_L \left(\frac{V_X}{V_{sat}} - 2 \right)$$

$$R_C \leq 3.750k\Omega$$

$$I_C = \frac{V_X}{R_C + (R_C || R_L)} = 0.6mA$$

$$R_B = \frac{V_{CC}}{N I_C} = 52.9k\Omega$$

$$R_E = \frac{V_E}{I_C} = 1.6k\Omega$$

$$R_G = \frac{1}{\left(\frac{R_C || R_L}{A_v} - R_E \right)} = 25.12\Omega$$

$$g_m = \frac{I_C}{V_E} = \frac{1mA}{25mV} = 0.04$$

$$V_B = 5 \left(\frac{27.25k}{27.25k + 52.9k} \right) = 1.6999$$

$$r_e = 25$$

$$I_{supply} = \frac{5 - 1.7}{52.9k\Omega} + 0.6mA \approx 0.66mA$$