

[illegible]

Lab # 2

find V_{E4} st. $V_{E4} + V_{E3, sat} \leq V_{E3} - V_{sat, diode peak}$

$$V_{E4} + 0.2 \leq V_{E3} - 1.5$$

$$0.5 + 0.2 + 1.5 \leq V_{E3}$$

$$2.2 \leq V_{E3}$$

$$R_{E3} = \frac{V_{E3}}{I_Q} = 33.3$$

$$I_Q \cdot R_{E3} = V_{CC} \frac{R_{B6}}{R_{B5} + R_{B6}} - 0.7$$

$$R_{B6} = 10k\Omega$$

$$R_{B5} = 5.625k\Omega$$

$$R_{in val} = \frac{R_{in}}{R_{in} + R_{rest}}$$

Lab #2


$$V_{CC} = 5V$$

$$|A| = 30$$


$$I_{supp} \leq 20mA$$

$$R_{in} \geq 3k\Omega$$

$$\beta = 190$$

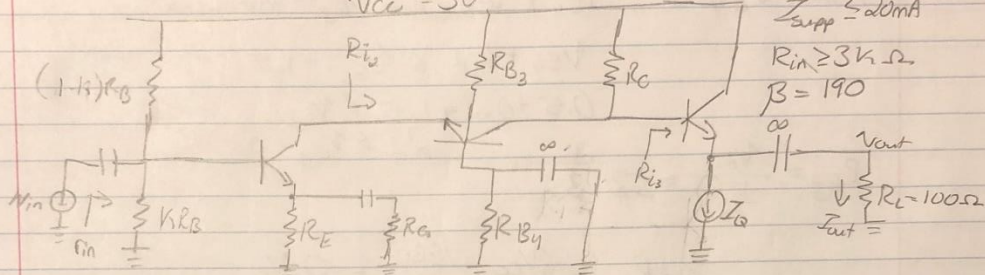
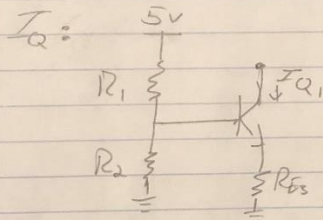
$$V_{E1} \geq 1V \quad V_{E4} \geq 0.5V \quad V_{swing} \geq 1.5V \quad \text{Operation frequency} = 5kHz$$



$$I_Q \geq \frac{1.5V}{100\Omega} = 15mA$$

$$I_{C3} = I_Q \Rightarrow A_F = \frac{V_{out}}{V_{in}} = \frac{R_L}{R_{E3} + R_L} = 0.98$$

$$g_m = \frac{I_{C3}}{V_T} = 0.6 \quad r_{E3} = 1.667$$

$$R_{i3} = (\beta + 1)(R_{E3} + R_L) = 19.418k\Omega$$

$$V_{E1} = 1V$$

$$V_{Ea} \geq V_{E1} + V_{CE,sat} + v_{i,max} \Rightarrow 1V + 0.2V + \frac{1.5}{30} \geq 1.25$$

$$V_{Ea} = 1.25V$$

$$V_X = V_{CC} - V_{E1} - V_{CE,sat} = 3.3V$$

$$K = \frac{(V_{E1} + 0.2)}{V_{CC}} = 0.34 \quad N = 10$$

$$R_C \geq (\beta R_{i3} - R_{ind} \frac{A_V}{A_F}) + R_C (2\beta R_{i3} - 3R_{ind} \frac{A_V}{A_F} - QR_{ind}) - R_{E3}^2 R_{ind} (Q + 2 \frac{A_V}{A_F}) \geq 0$$

$$Q = \frac{N_{max}}{K(1 - K)V_{CC}} \quad \min R_C = 5.39k\Omega$$

$$R_C \leq R_{i3} \left(\frac{V_X A_F}{V_{E1}} - 2 \right) = 6.366k\Omega$$

$$R_C = 6k\Omega$$

$$I_{C1} = I_{C2} = \frac{V_X}{R_C + (R_C \parallel R_{i3})}$$

$$R_B = \frac{\beta V_{CC}}{V_{E1}} = 28k\Omega$$


$$R_E = \frac{V_E}{I_{C1}} = 2.98k\Omega$$

$$R_G = \frac{1}{\frac{R_C \parallel R_{i3} A_F - R_{E1}}{A_V} - \frac{1}{R_E}} = 77.72\Omega$$

$$g_{m1} = \frac{I_{C1}}{V_T} = 0.0134$$

CIRCUIT:

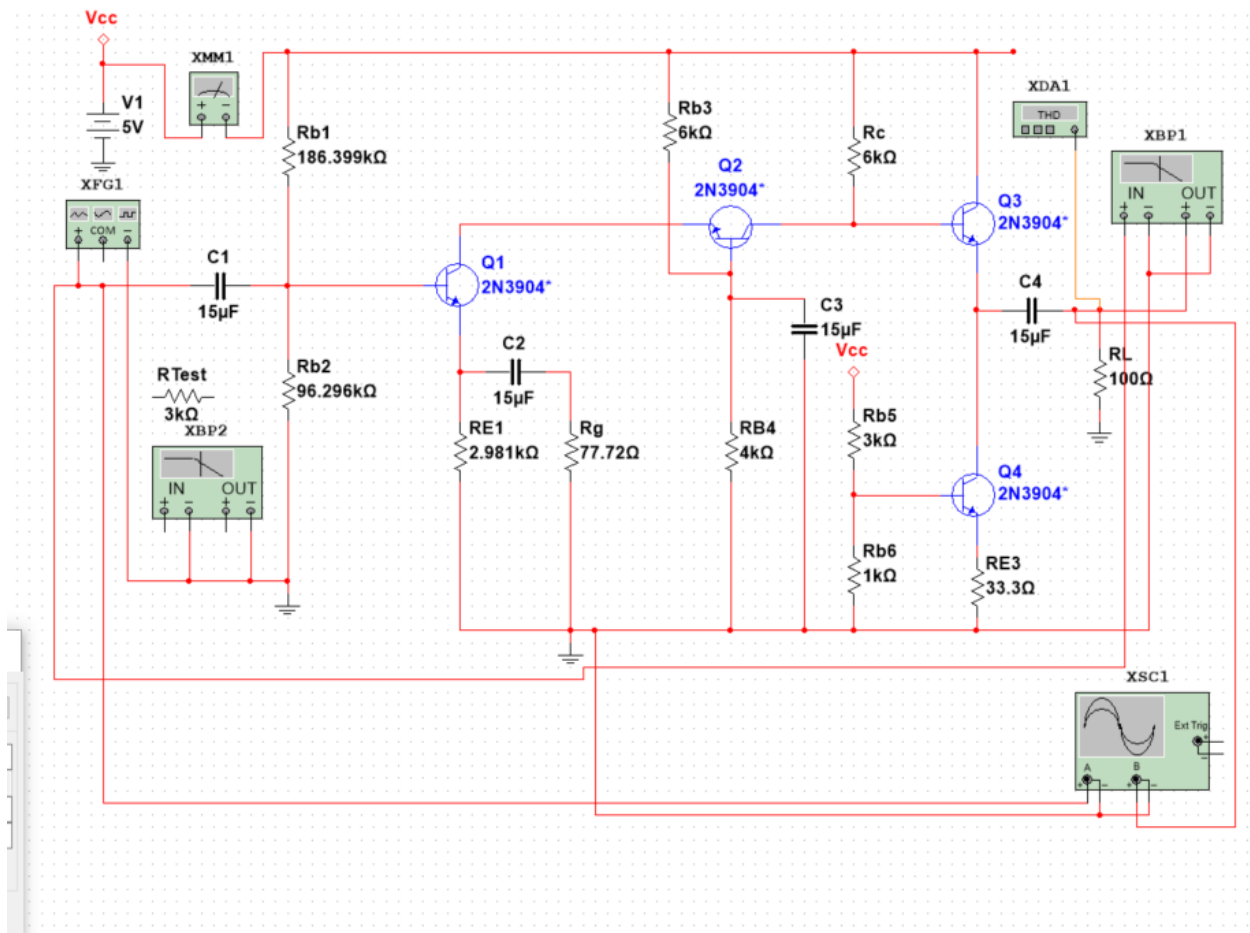Below is the circuit used for both the simulations and measurement data collected:




SIMULATION PLOTS:


DC Operation Points:

	Variable	Operating point value
1	I(Q1:C) I(Ic1)	-283.99462 u
2	I(Q2:C) I(Ic2)	-280.69519 u
3	I(Q3:C) I(Ic3)	12.47339 m
4	I(Q4:C) I(Ic4)	12.59009 m
5	V(1) V(Vb1)	1.48957
6	V(5) V(Vb2)	1.99208
7	V(2) V(Vb3)	2.61567
8	V(9) V(Vb4)	1.15949
9	V(8) V(Vc1)	1.35969
10	V(2) V(Vc2)	2.61567
11	V(vcc) V(Vc3)	5.00000
12	V(3) V(Vc4)	1.88042
13	V(7) V(Ve1)	856.61648 m
14	V(8) V(Ve2)	1.35969
15	V(3) V(Ve3)	1.88042
16	V(10) V(Ve4)	423.26830 m
17	V(4) V(Vout)	0.00000e+00

Gain:

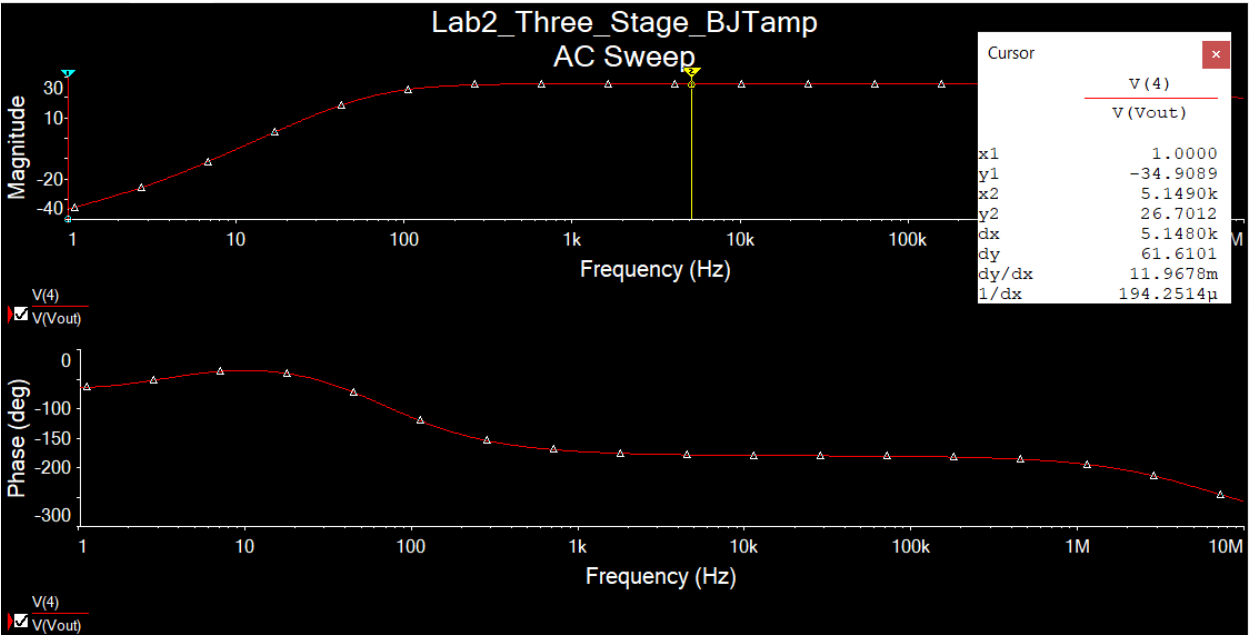


Rin:

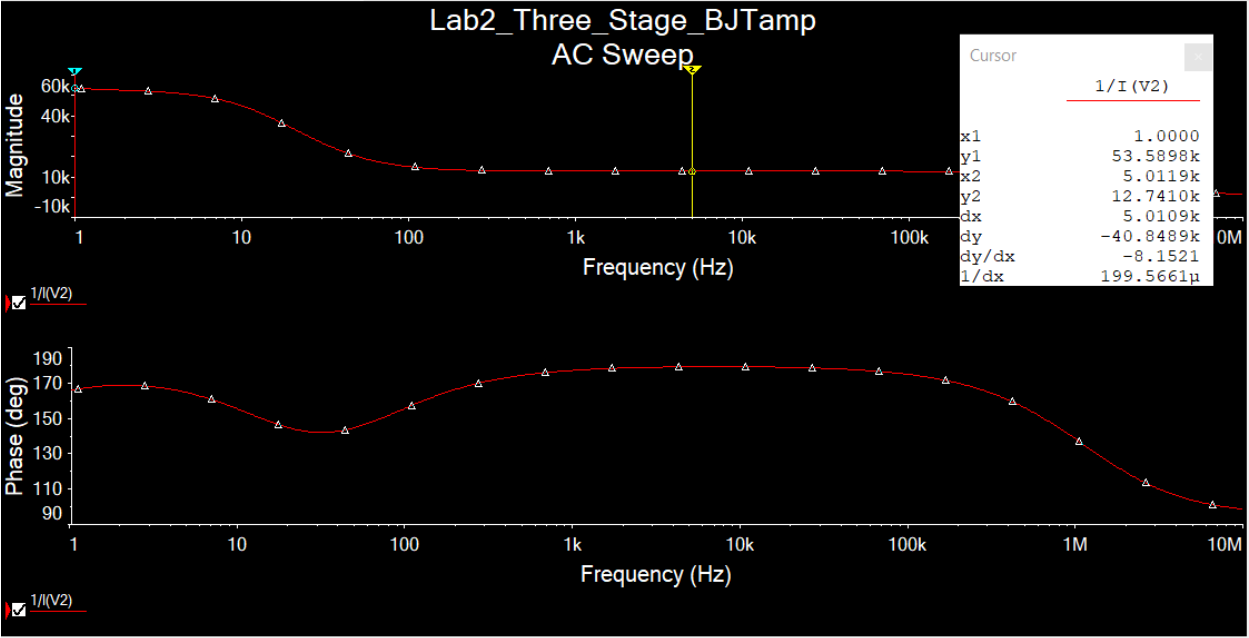


Isupply:

	Variable	Operating point value
1	-I(V1:1)-I(Rb5:1) I(PR1)	13.39093 m

THD:

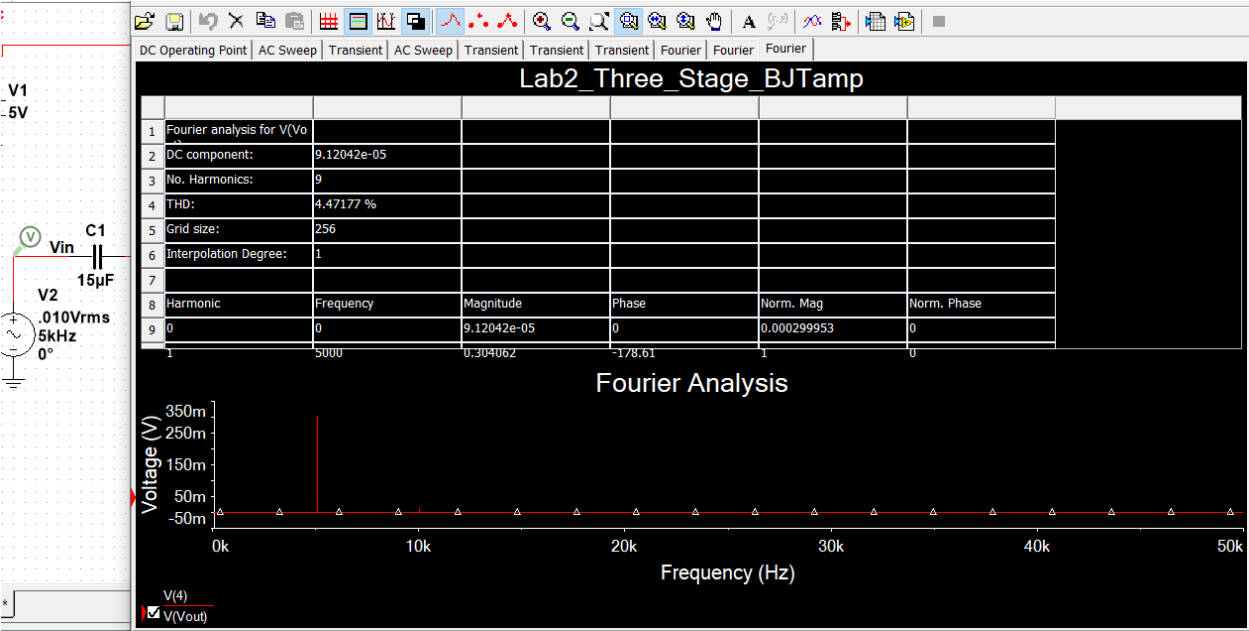


Waveform:

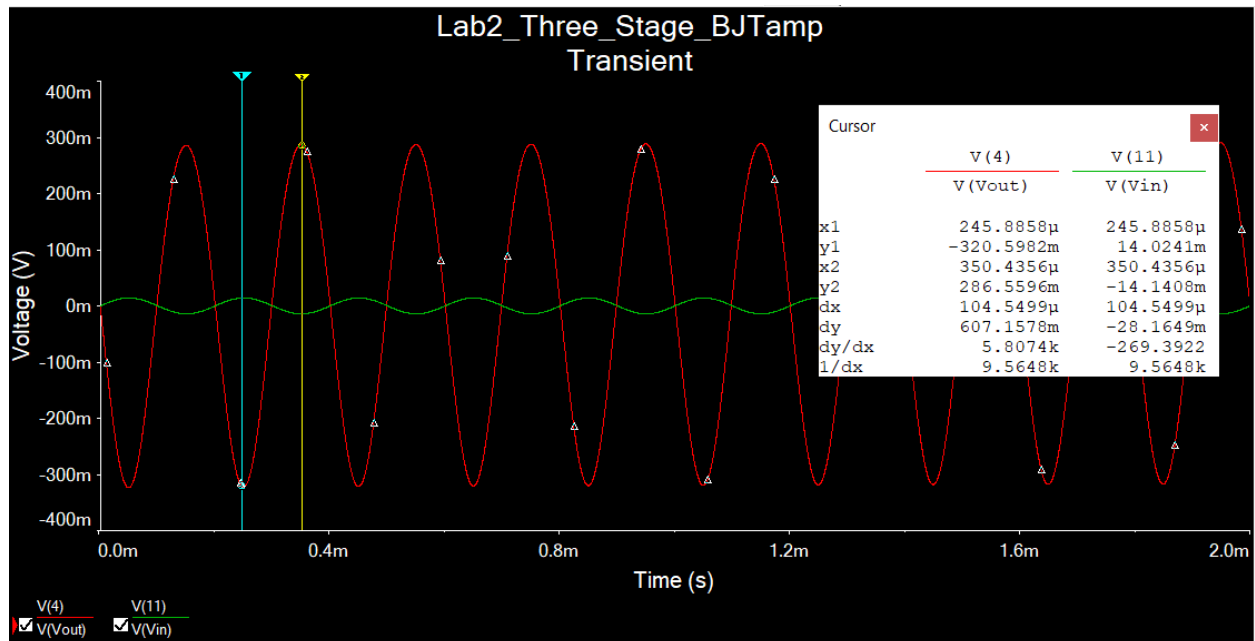



MEASUREMENT PLOTS:


DC Operation points of the relevant information shown below:

Q1:

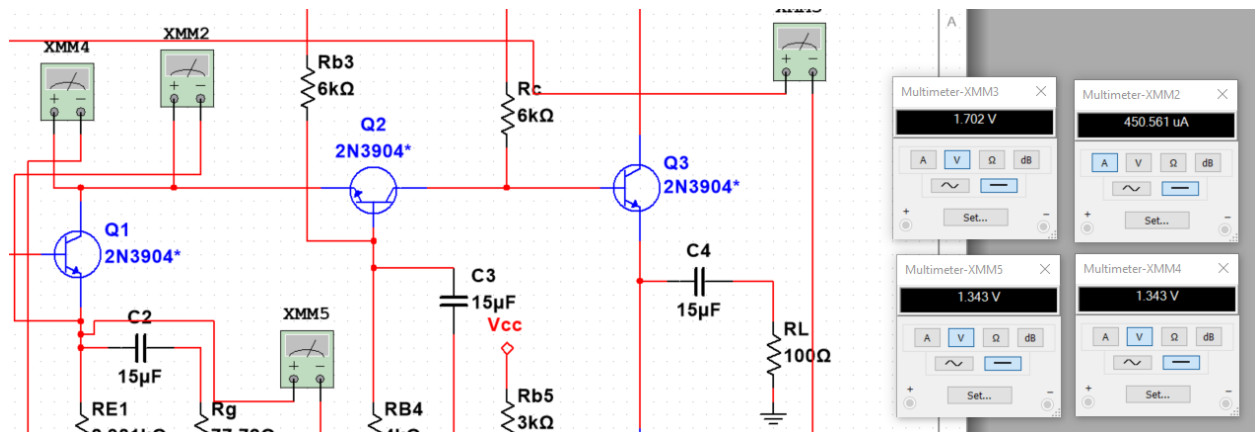


Q2:

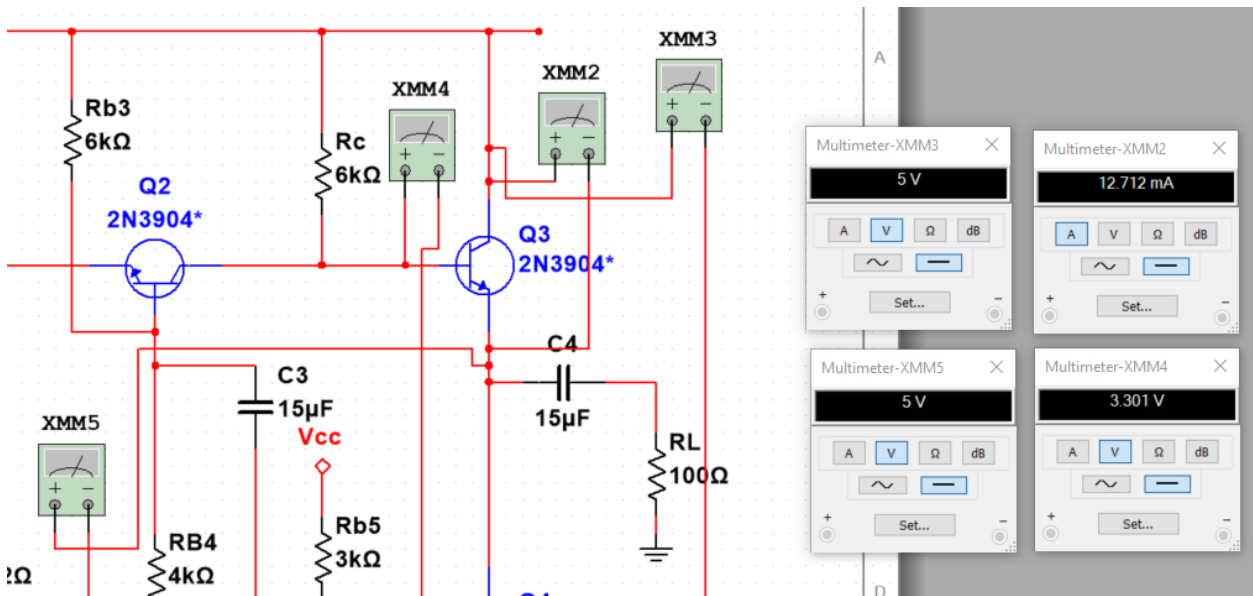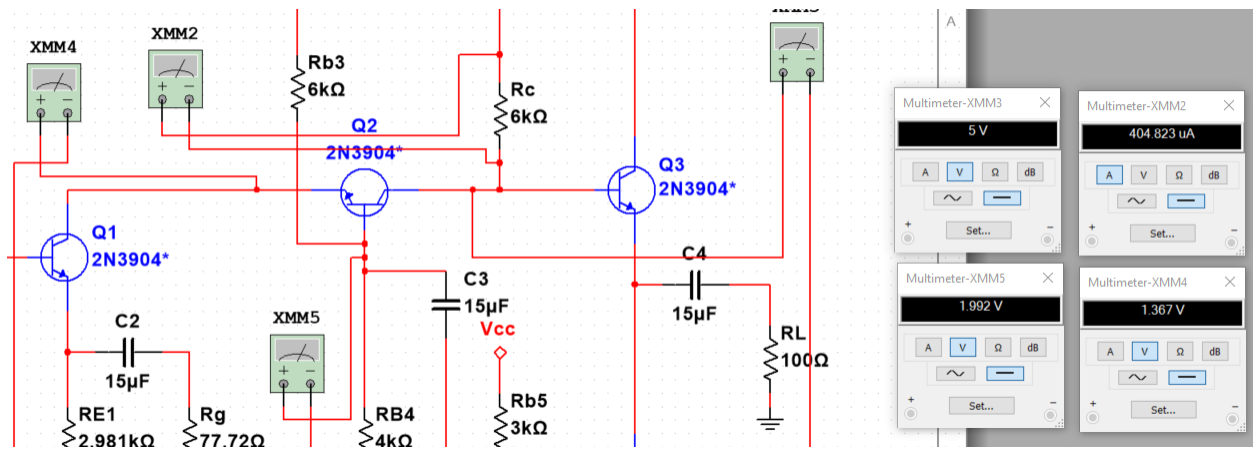

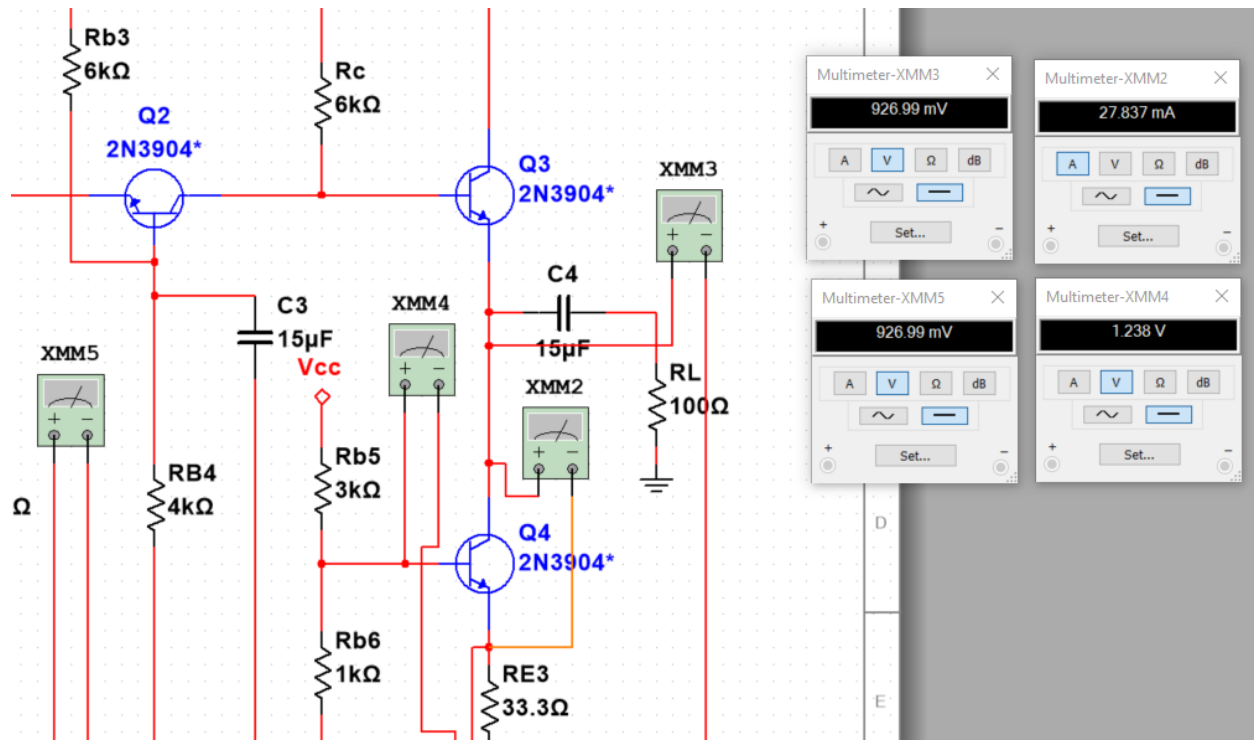


The gain is shown below:

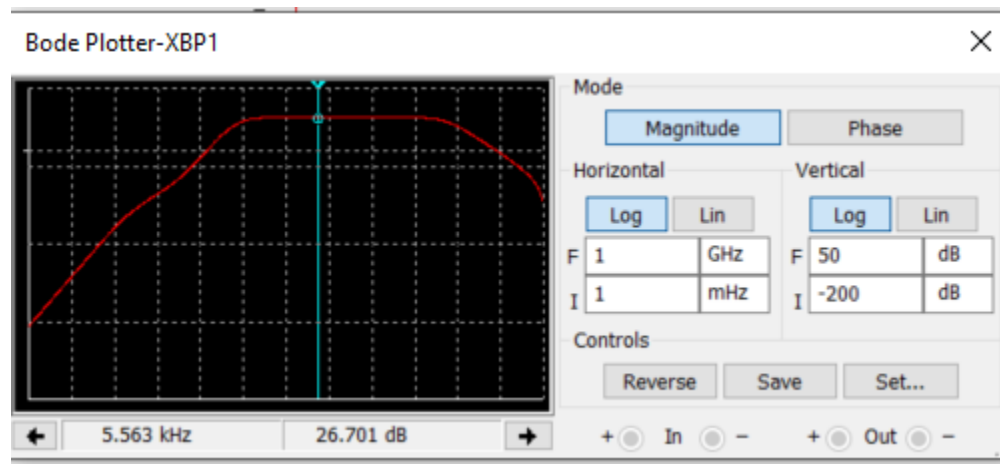


The gain is 26.7 dB

The measurement for Rin is shown below:

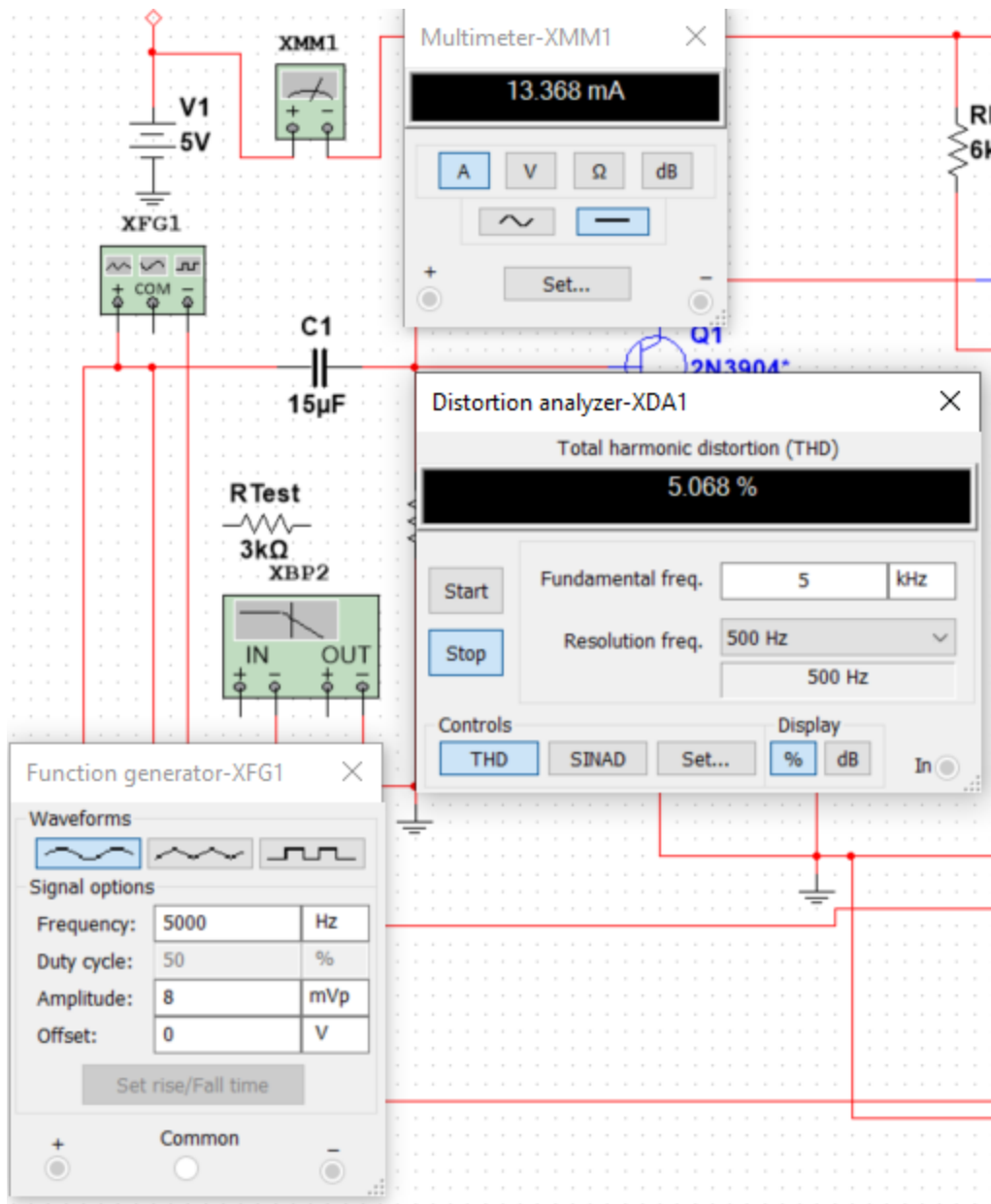

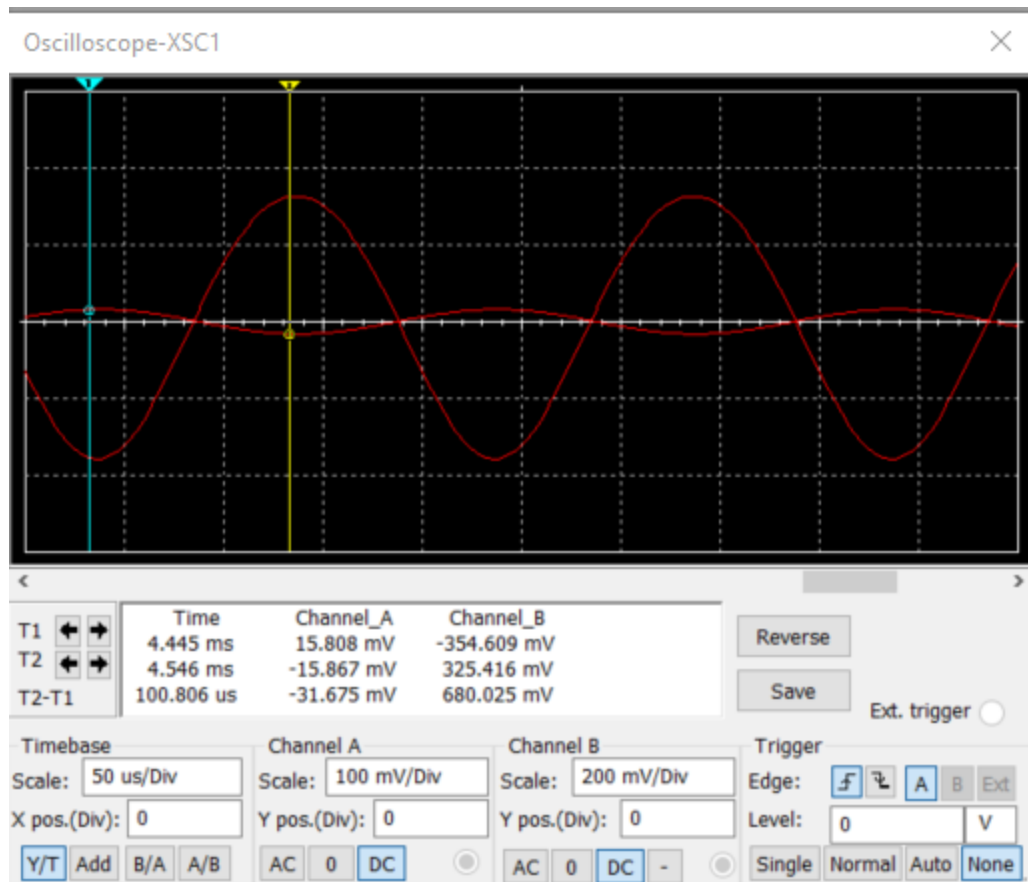
Below is the resultant oscilloscope information given the above information



This is the signal amplitude that resulted from the 5% THD shown in the previous data above. The peak-to-peak swing voltage is approximately 0.7 volts.

Below is the maximum unclipped voltage and relevant waveform information:

Oscilloscope-XSC1

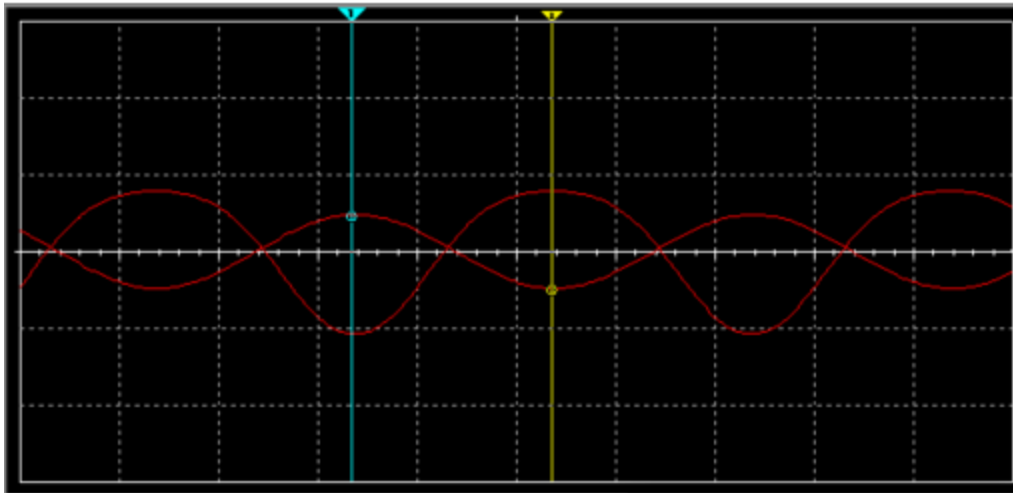

T1	← →	Time	Channel_A	Channel_B
T2	← →	33.248 ms	47.896 mV	-1.064 V
T2-T1		33.349 ms	-47.949 mV	789.646 mV
		100.806 us	-95.844 mV	1.853 V

Timebase		Channel A		Channel B	
Scale:	50 us/Div	Scale:	100 mV/Div	Scale:	1 V/Div
X pos.(Div):	0	Y pos.(Div):	0	Y pos.(Div):	0

<input checked="" type="button" value="Y/T"/>	<input type="button" value="Add"/>	<input type="button" value="B/A"/>	<input type="button" value="A/B"/>	<input type="button" value="AC"/>	<input type="button" value="0"/>	<input checked="" type="button" value="DC"/>
---	------------------------------------	------------------------------------	------------------------------------	-----------------------------------	----------------------------------	--

Function generator-XFG1




Waveforms



Signal options

Frequency:	5000	Hz
Duty cycle:	50	%
Amplitude:	24	mVp
Offset:	0	V

Set rise/Fall time

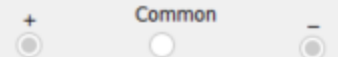

Results Analyzed

	Calculated	Simulated	Measured
Vc1	1.25volts	1.3569 v	1.343v
Vc2	2.0125volts	2.6156 v	2.516v
Vc3	5volts	5 v	5v
Vc4	2.2volts	1.88 v	926mv
Vb1	1.7volts	1.4895 v	1.702v
Vb2	2volts	1.99 v	1.992v
Vb3	2.0125volts	2.615 v	3.301v
Vb4	1.25volts	1.159 v	1.238v
Ve1	1volt	0.856 v	1.343v
Ve2	1.25volts	1.3596 v	1.367v
Ve3	2.2volts	1.8804 v	2.6v
Ve4	0.55volts	0.423 v	926mV
Ic1	335uA	283uA	450uA
Ic2	335uA	280uA	404uA
Ic3	14.665mA	12.47mA	12.712mA
Ic4	15mA	12.59mA	27.837mA
Isupply	20mA	13.3903mA	13.368mA
Av	30dB	26.7012dB	26.701dB
Rin	3k Ω	12.741k Ω	12.706k Ω
Output Swing @ 5%	1.5volts	0.606volts	0.680volts

The above data is representative of the circuit operating to produce a gain that is slightly smaller than the required for this lab. The small gain leads to the smaller output swing which is almost half of the value required. These differences are most likely due to poor design choices on my initial base resistors being much higher than they need to be. A point of difference can also be found on the collector voltage for the fourth BJT. This value is most likely to Multisim doing something weird with the capacitor on the branch and causing the value to fluctuate wildly. The value should be 0.7 volts lower than the base voltage on BJT 3 however it's not close.