

Matthew Loden


Lab 5: Design of a MOS Differential Amplifier

Purpose:

In this lab, we will create a MOSFET differential amplifier and determine the CMRR from it. We will also study the differences between this MOS design and last weeks BJT design.

Calculations:

Lab #5

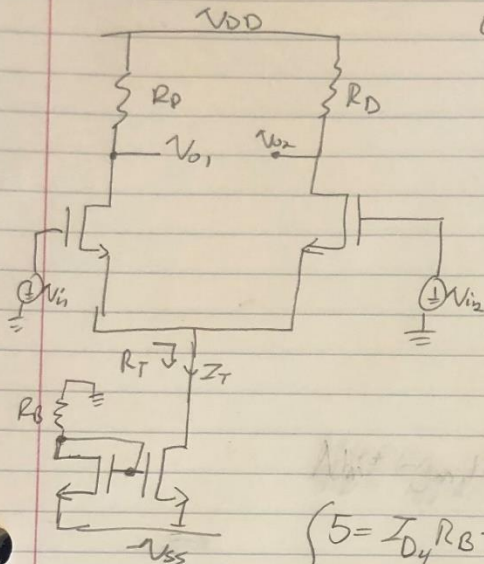

using CD407N
 $K'_n = 70 \mu A/V^2$
 $V_{tn} = 1.4V$
 $W = 170 \mu m$
 $L = 10 \mu m$
 $\lambda_n = 0.016 V^{-1}$

Constraints

$V_{ic} = 0V$ $I_{supply} \leq 0.5mA$
 $V_{DD} = V_{SS} = 5V$ $|A_{dm}| \geq 10$
 $THD \leq 5\%$ for $5V$ utpeak @ $1kHz$

$$\begin{cases} 5 = I_{D4} R_B + V_{GS4} \\ I_{D4} = \frac{K'_n}{2} \frac{W}{L} (V_{GS4} - V_{tn})^2 \\ 10 = \sqrt{2 K'_n \frac{W}{L} \frac{I_{D4}}{2}} \end{cases}$$


$$R_D = 200 k\Omega$$

$$V_{GS} = 2V$$

$$I_{D4} = 35 \mu A$$

$$I_{D1} = 17.5 \mu A$$

Circuit:

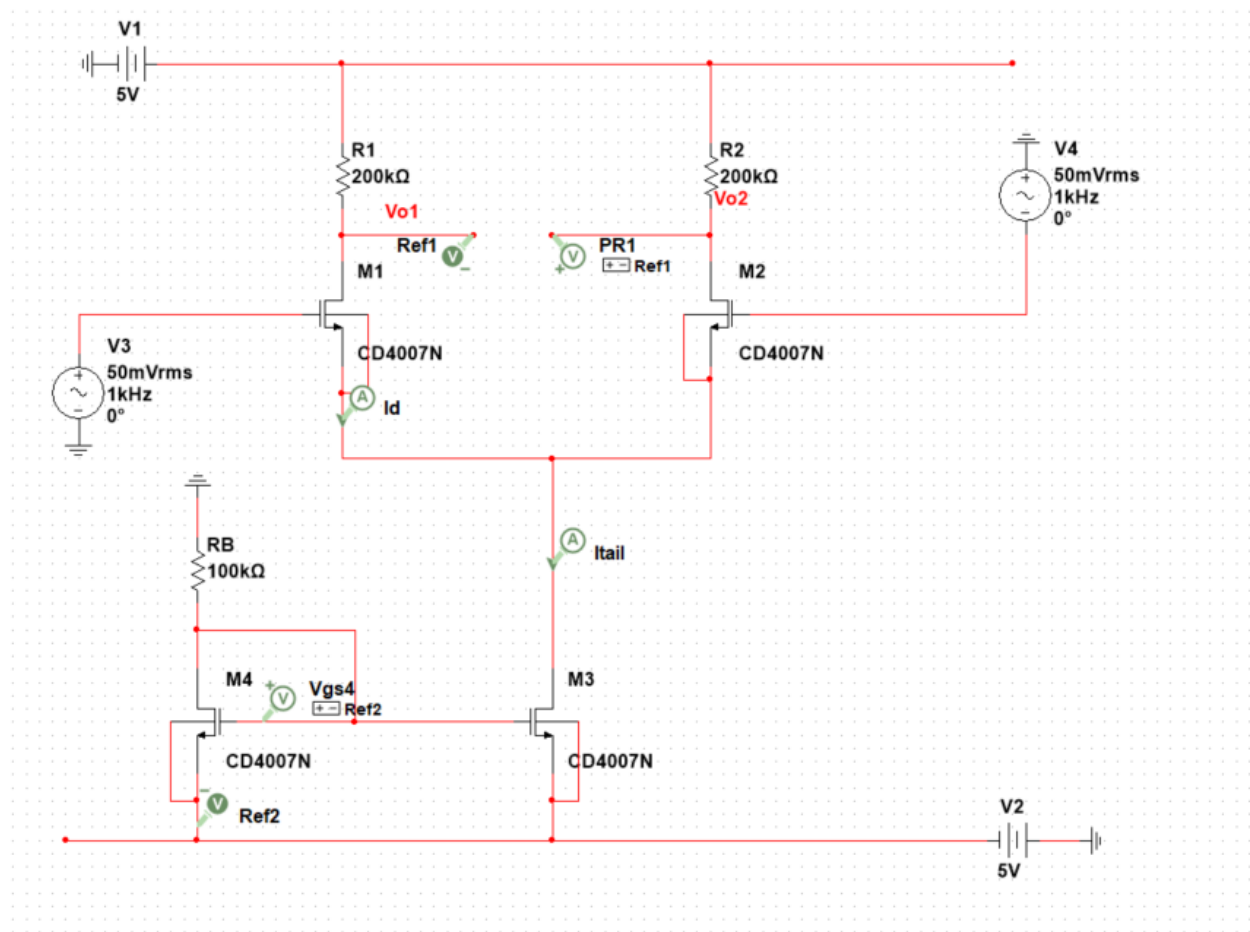


Simulations:

DcOp:


	Variable	Operating point value
1	$-I(vM1.PinVoltageS--4:S)-I(vM1.PinVoltageSUB--4:SUB) \mid I(Id)$	17.97058 u
2	$I(vM3.PinVoltageD--4:D) \mid I(Itail)$	35.94116 u
3	$V(vo2) - V(vo1) \mid V(PR1)$	0.00000e+00
4	$V(3) - V(1) \mid V(Vgs4)$	1.61655

Aid:

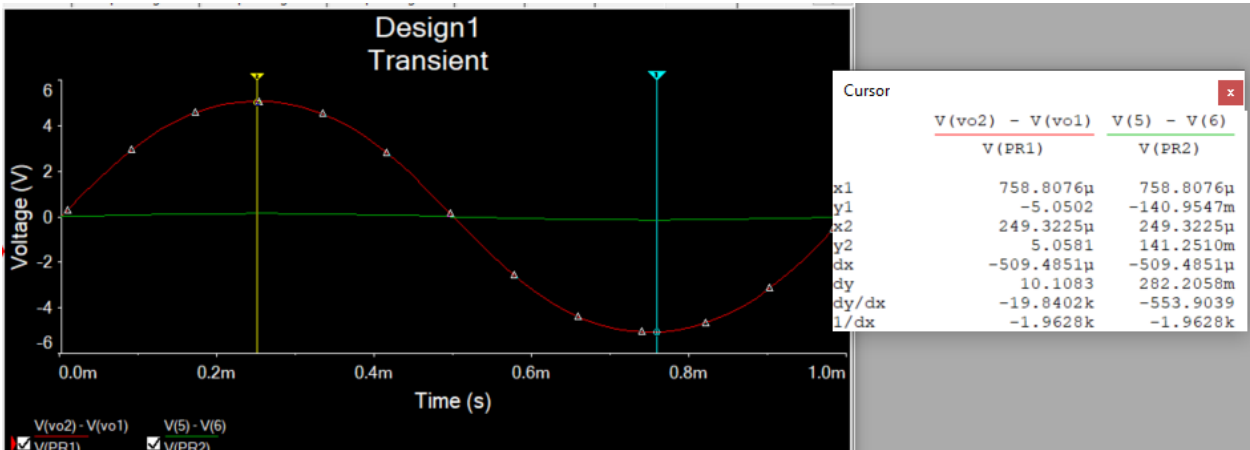


$= 10 / .282 = 35.46$

Aic:

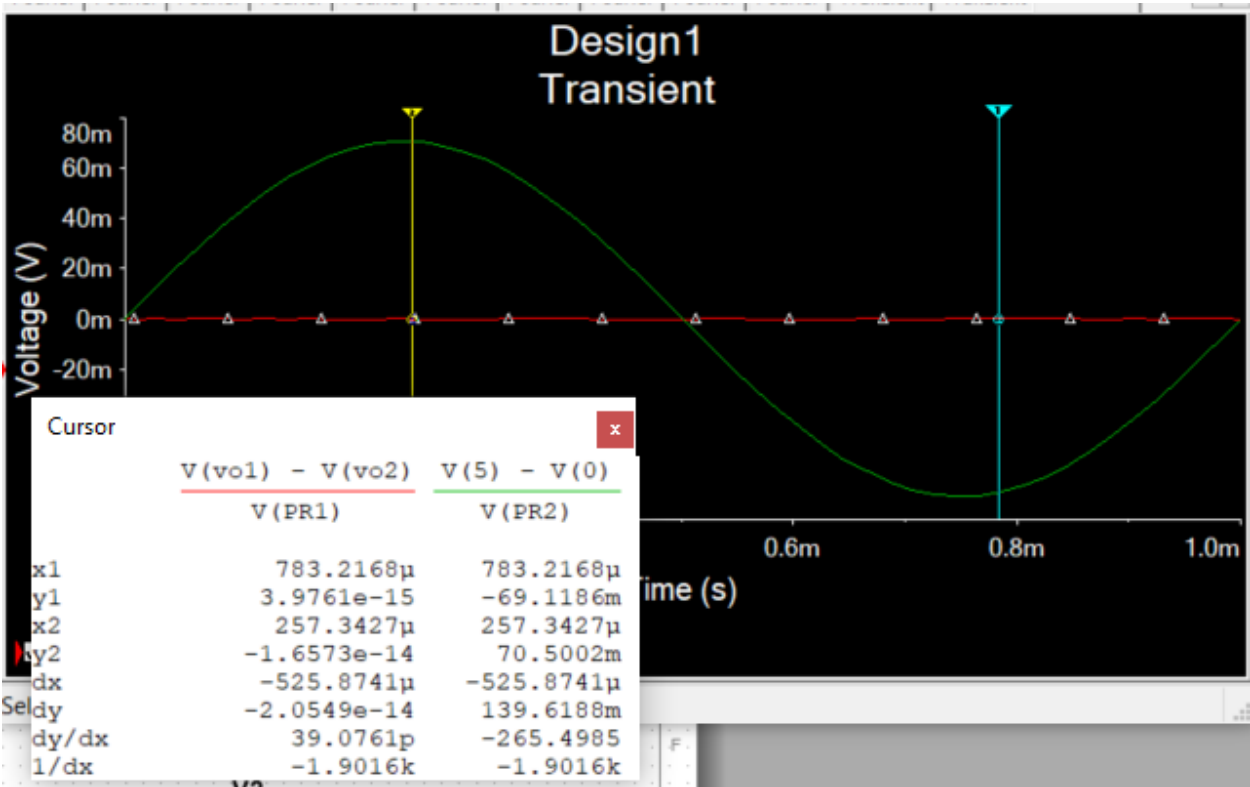


$= 2.054e-14 / .139 = 1.47e-13$

THD:

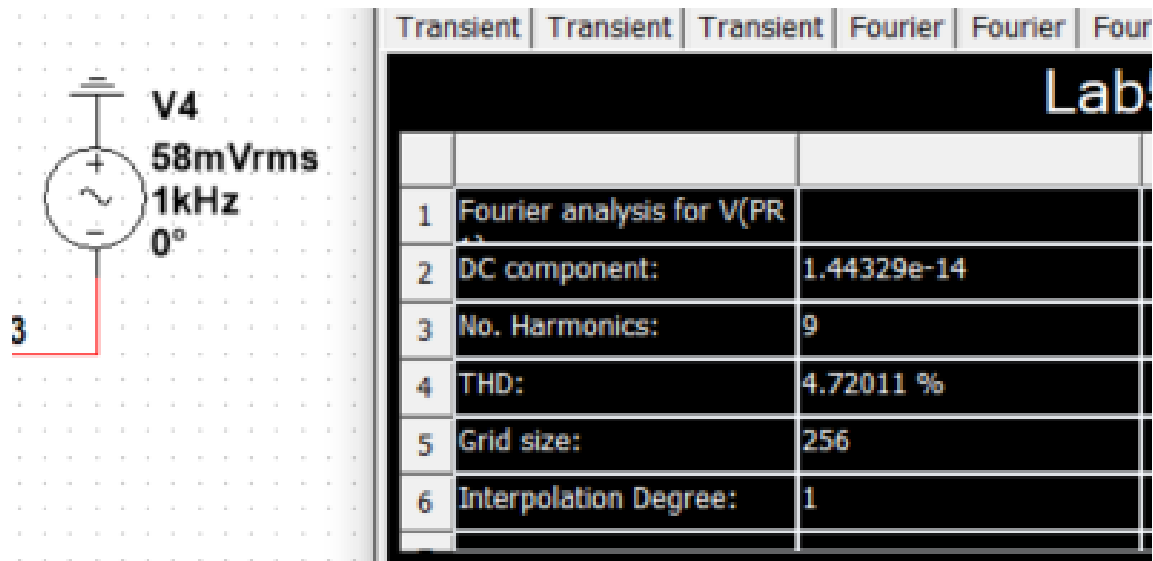


Measurements:


DcOp:

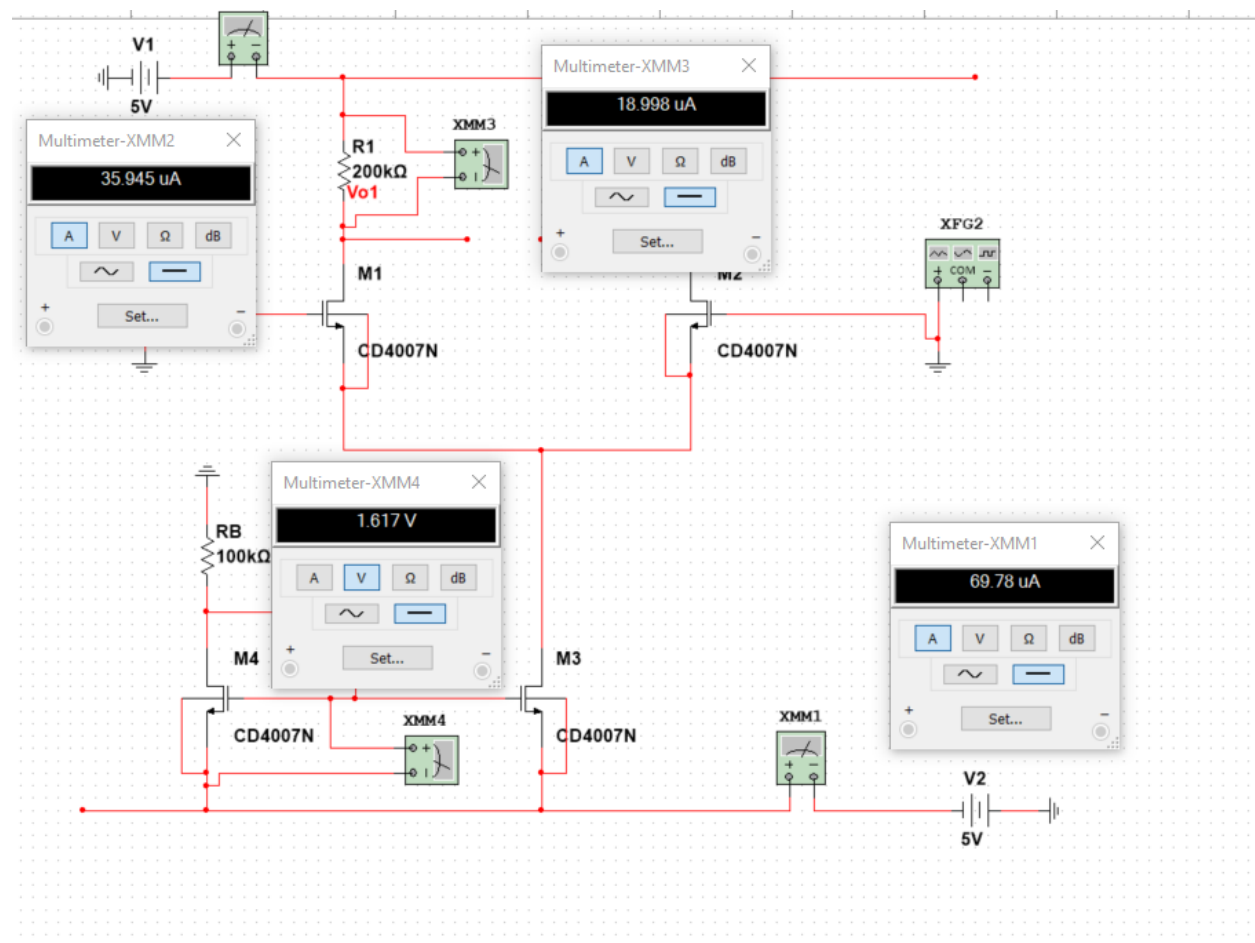

Vov:

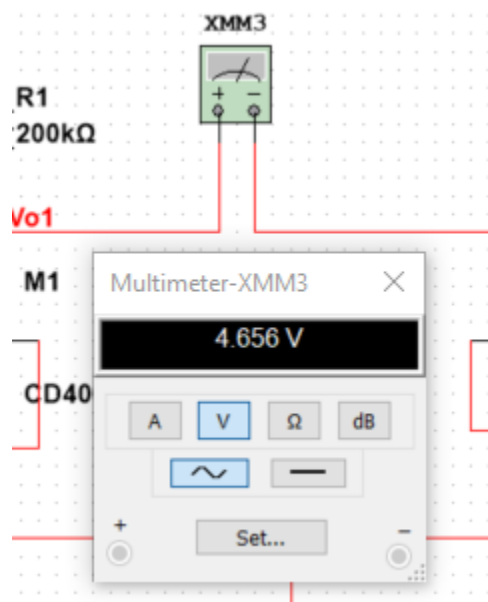


Adm:

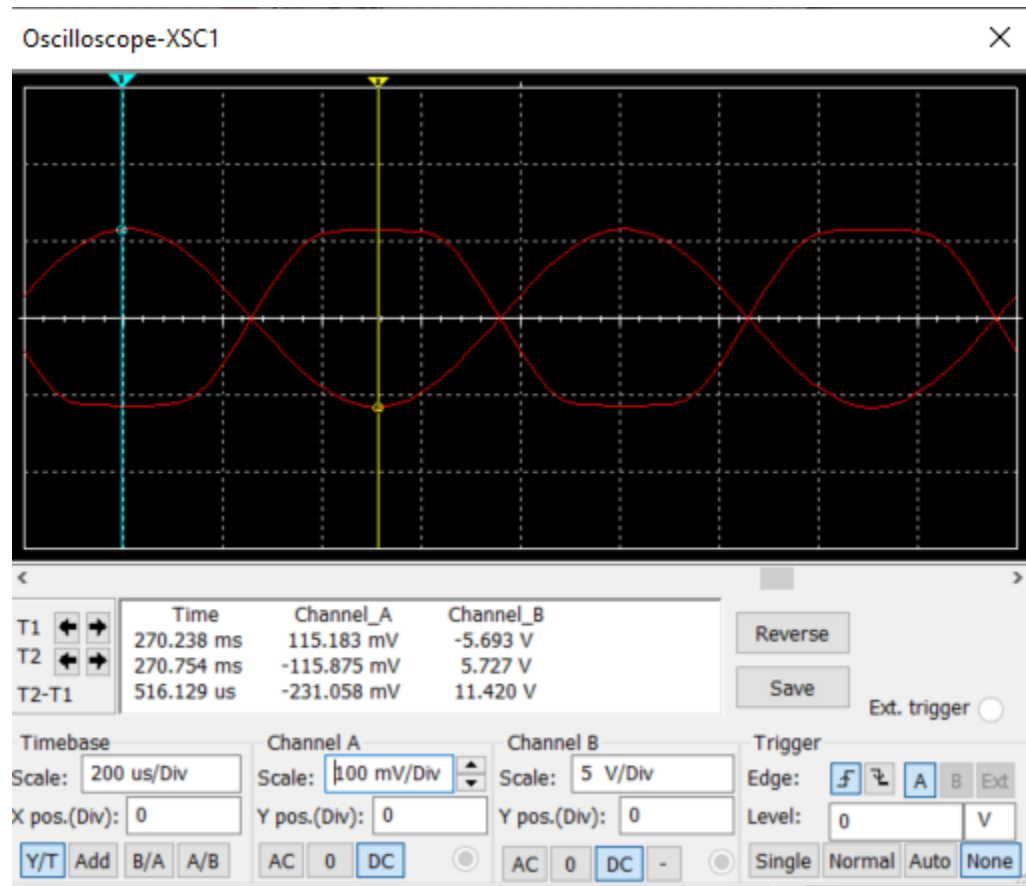


$$= 11.420 / 0.231 = 49.43$$


0 to 5 volt peak to peak

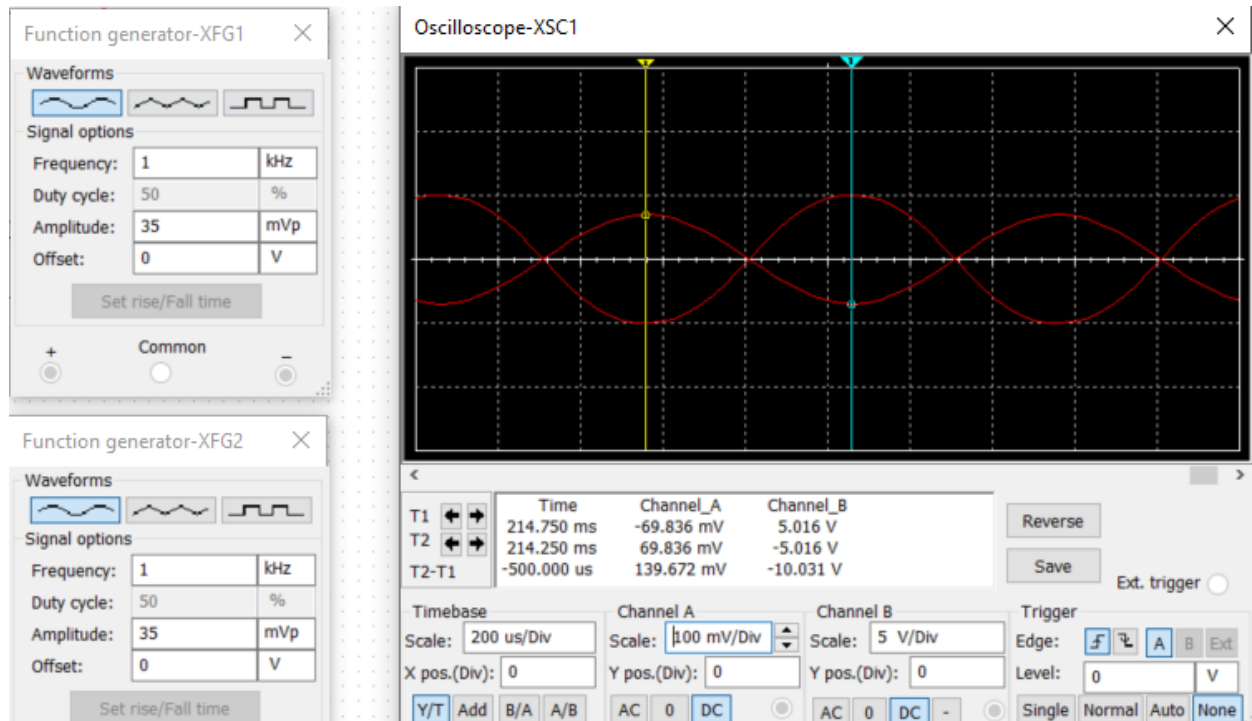

THD at this value

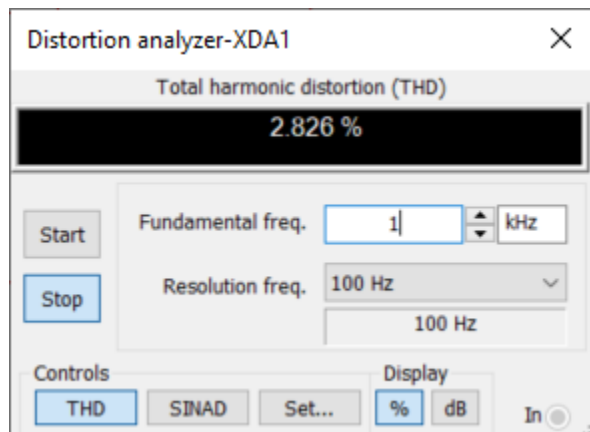

Acm:

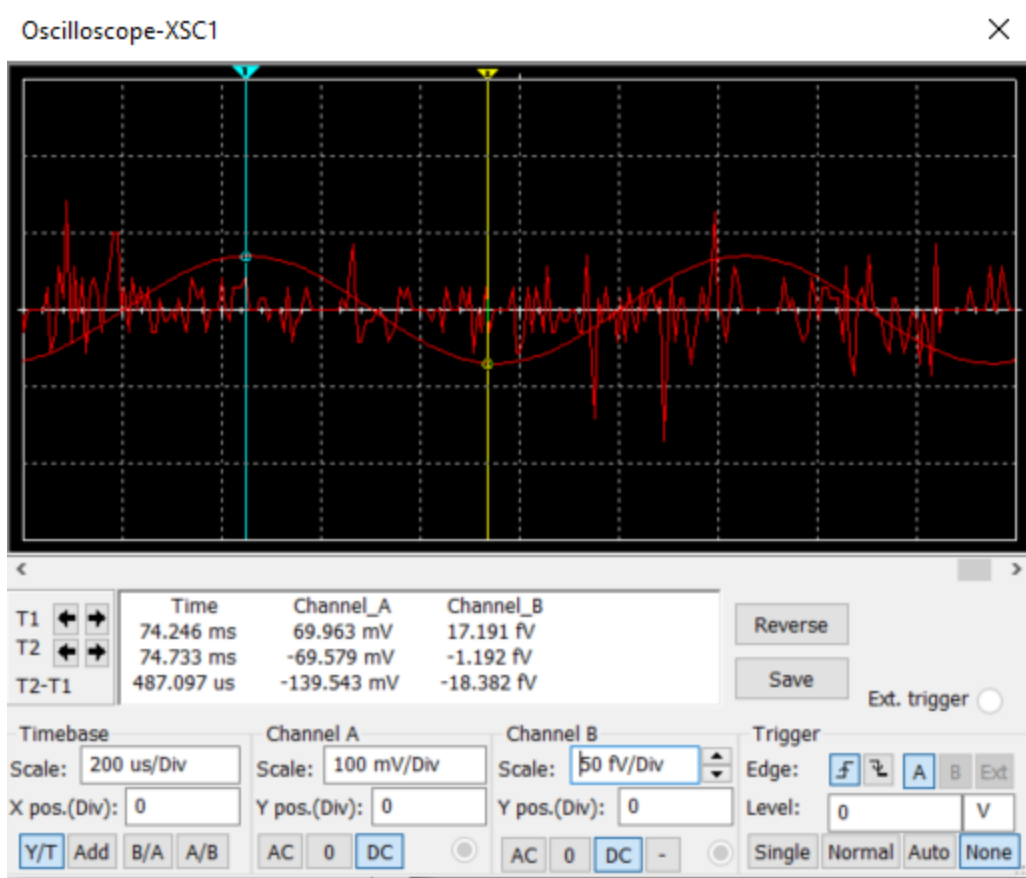

CMRR: -197.75dB

Results Explained:

	Calculations	Simulations	Measurements
Vgs4	2v	1.61v	1.617v
Itail	35uA	35.94uA	35.945uA
Id	17.5uA	17.97uA	18.998uA
Aid	>10	35.46	49.43
Isupply	<500uA	35.94uA	35.945uA

As you can see, all of my simulated values closely match my measurement values. The biggest differences comes from the gain values however I used different input amplitudes to measure these different values to get the correct level of THD. The calculations are all met however my Vgs4 value is a little bit off.