

Matthew Loden

ECEN 326 – 501


Lab 10: Design of a BJT Feedback Amplifier

Purpose:

This lab is used to determine the effects of adding a feedback component to a cascade BJT amplifier design. This will allow us to greatly increase the gain of the system with different side effects. We will study these differences from the previous labs.

Calculations:

Lab # 10

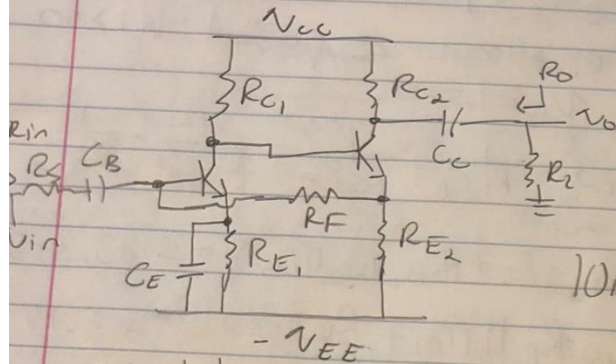

$$V_{CC} = V_{EE} = 5V$$

$$R_S = 50\Omega \quad R_L = 10K\Omega$$

$$V_{RE1} \geq 0.4V \quad I_{supply} = 10mA$$

$$|A_v| \geq 80 \quad V_{sw} \geq 3.5V$$

$$10mA = I_{C1} + I_{C2}$$

$$\therefore I_{C1} = 7.6mA$$

Calculations

$$V_{RE2} \approx V_{RE1} + 0.7 \Rightarrow V_{RE2} = 1.1V$$

$$V_{RC1} \approx V_{CC} + V_{EE} - V_{RE1} - 1.4$$

$$V_{RC1} \Rightarrow 8.2V$$

$$\left\{ I_{C2} = \frac{V_{CC} + V_{EE} - 2V_{RE2} - V_{CE,sat}}{R_{C2} + (R_{C2} \parallel R_L)} \right\} \Rightarrow 2.41mA$$


$$V_{SW} = \frac{V_{CC} + V_{EE} - 2V_{RE2} - V_{CE,sat}}{2 + \frac{R_{C2}}{R_L}} \Rightarrow R_{C2} = 1.7K\Omega$$

$$R_{E1} = \frac{V_{RE1}}{I_{C1}} = 52.63\Omega \quad R_{C1} = \frac{V_{RC1}}{I_{C1}} = 1.078K\Omega$$

$$R_{E2} = \frac{V_{RE2}}{I_{C2}} = 456\Omega$$


$$R_{C1} = \frac{25mA}{2.41mA} = 10.373$$
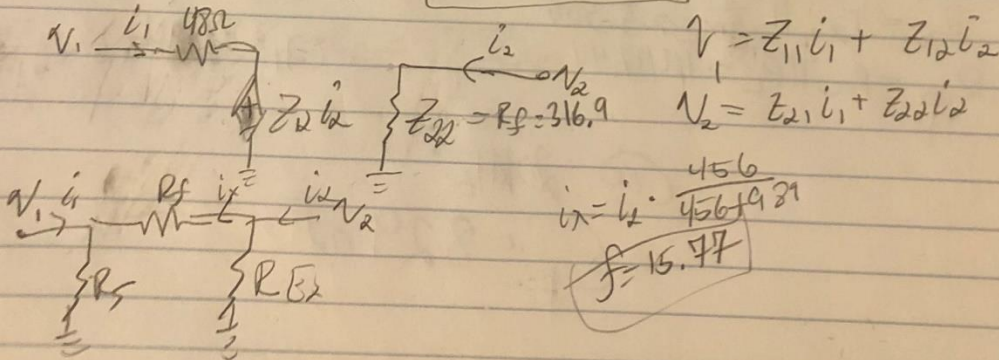
$$L \approx \frac{R_{C1}}{R_{C1}} \cdot \frac{R_S}{R_S + R_F} \Rightarrow R_F = 989\Omega$$



Simulations:


Circuit

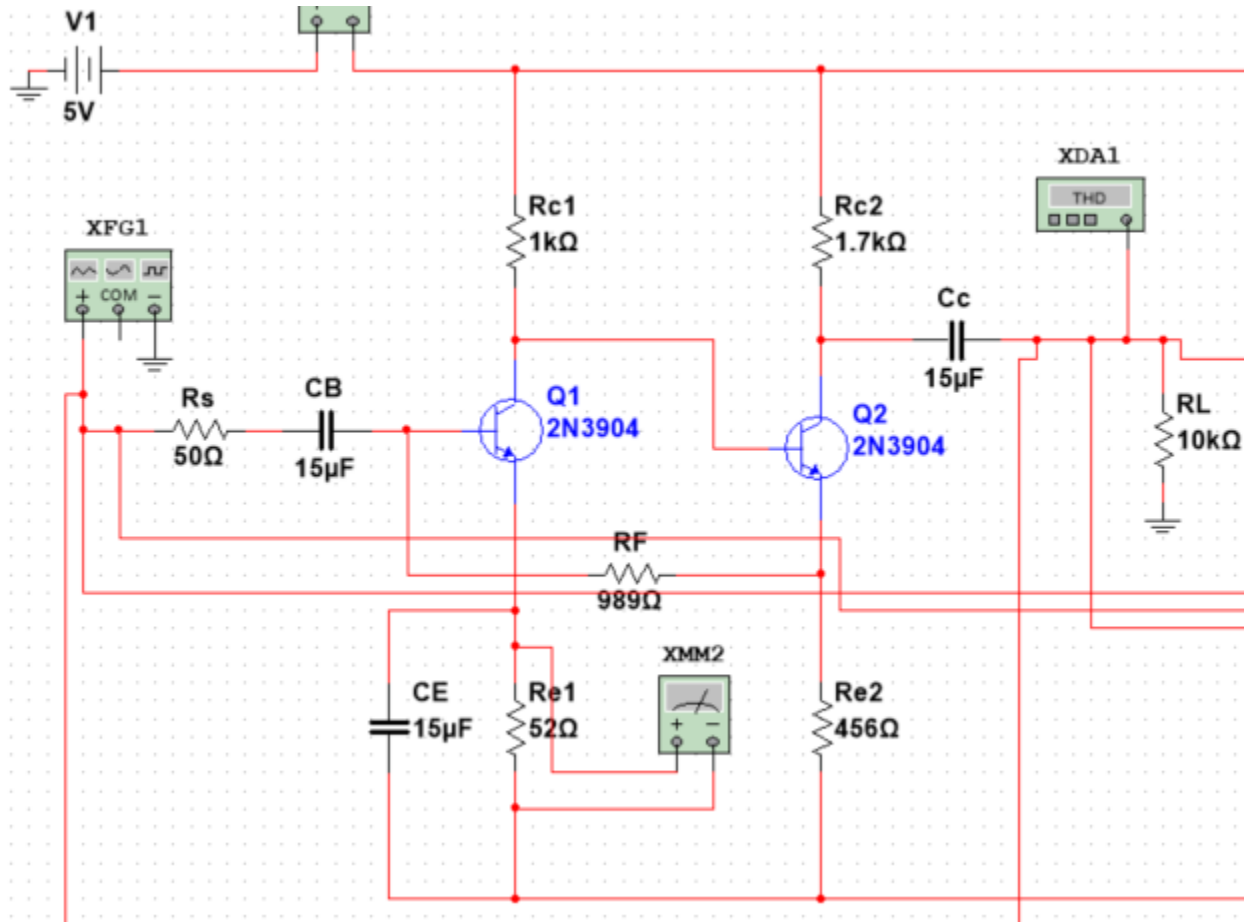


DcOp

	Variable	Operating point value
1	I(Rc1:1) I(Ic1)	7.57543 m
2	I(Rc2:1) I(Ic2)	2.54046 m
3	-I(XMM1:2) I(Isupply)	10.11589 m
4	V(2) V(Vb1)	-3.87907
5	V(1) V(Vb2)	-3.16631
6	V(1) V(Vc1)	-3.16631
7	V(5) V(Vc2)	681.21038 m
8	V(3) V(Ve1)	-4.59969
9	V(4) V(Ve2)	-3.85553


Gain

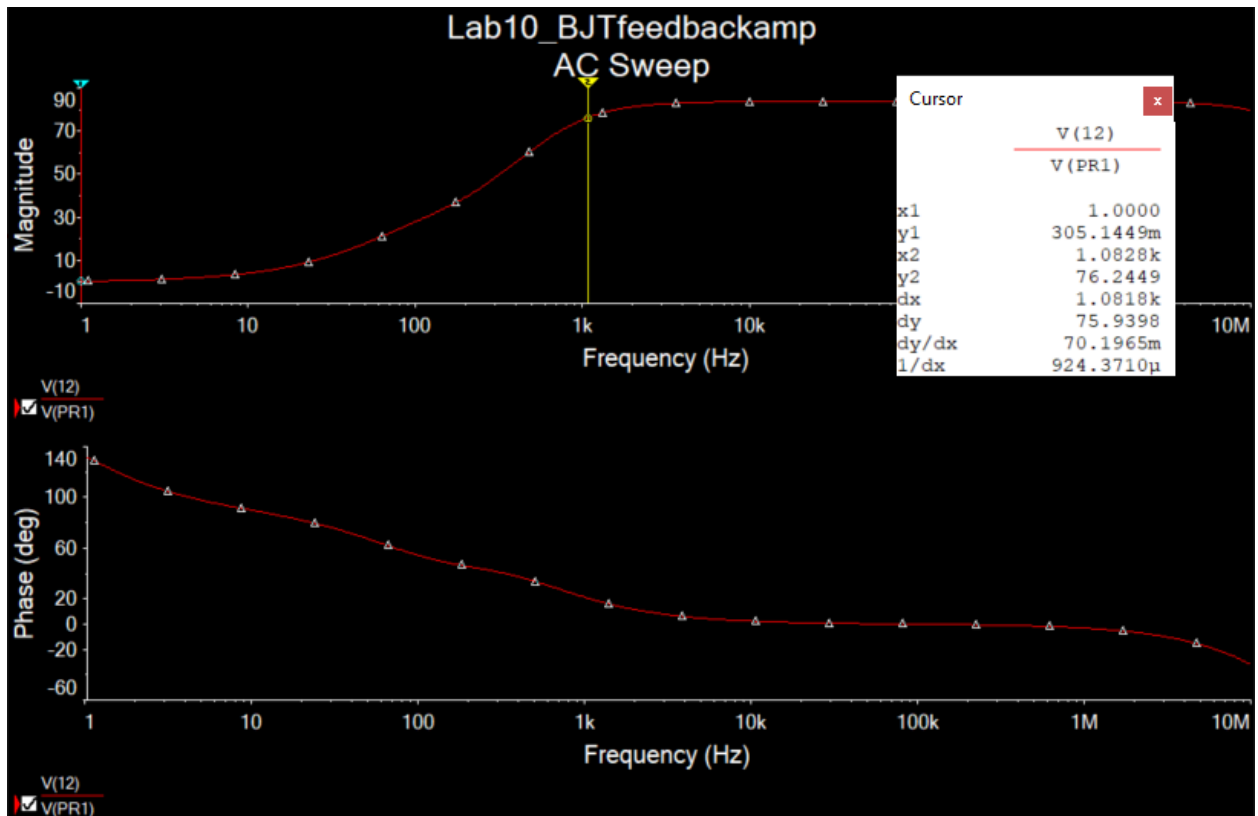


Ri

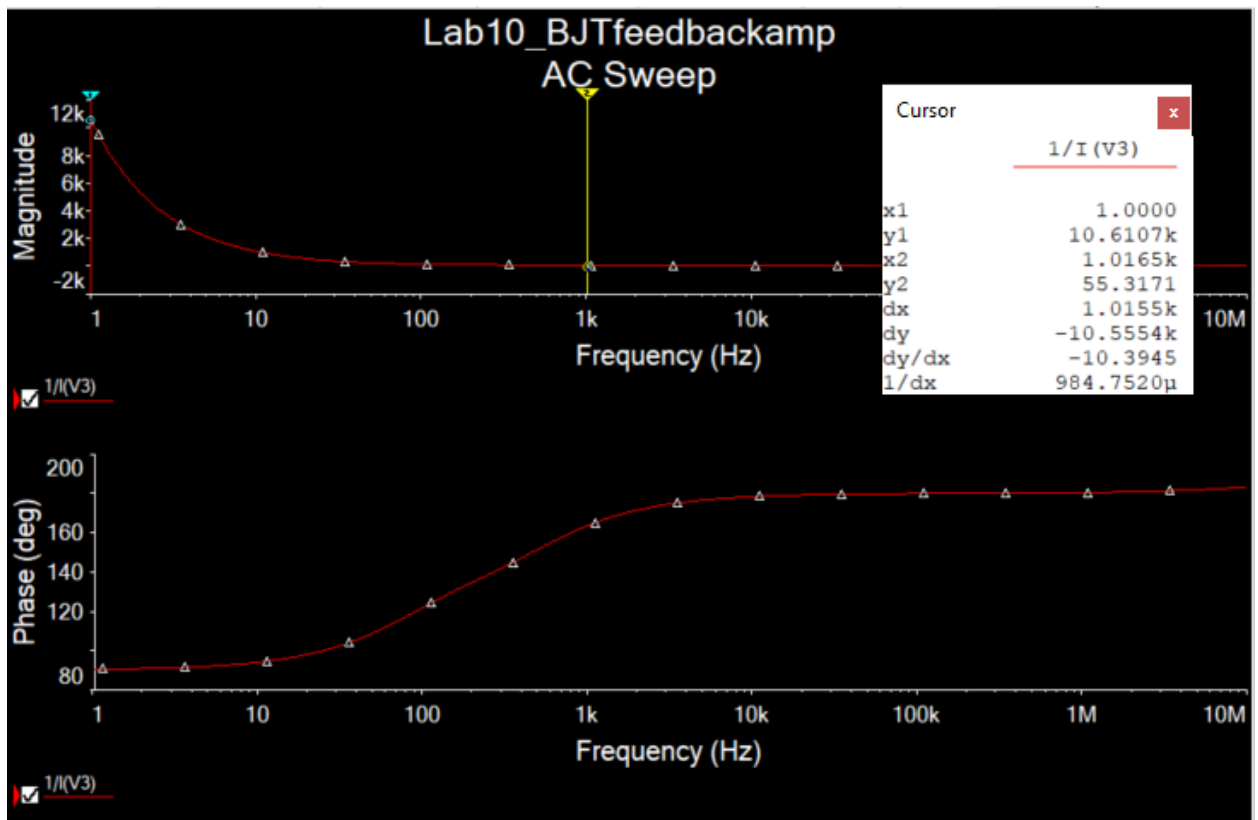


Ro

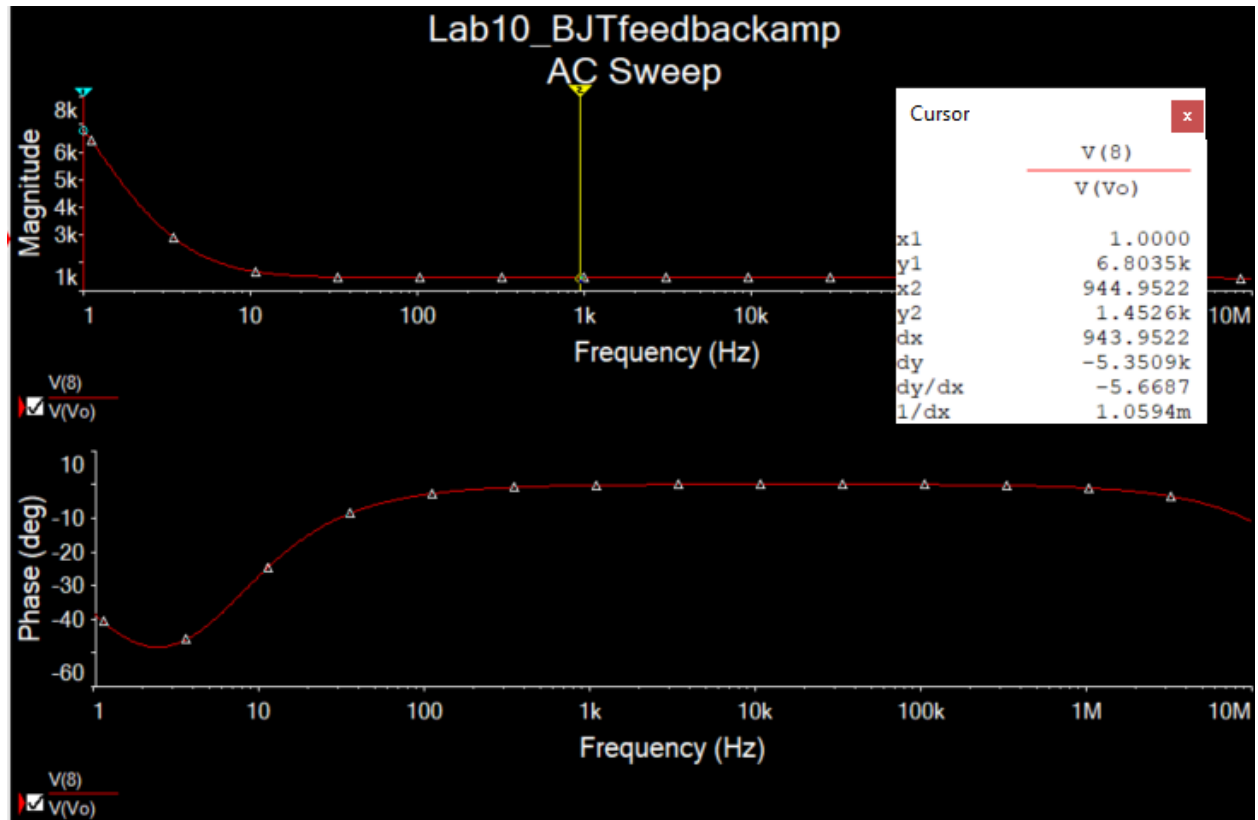

Unclipped output of 0-3v

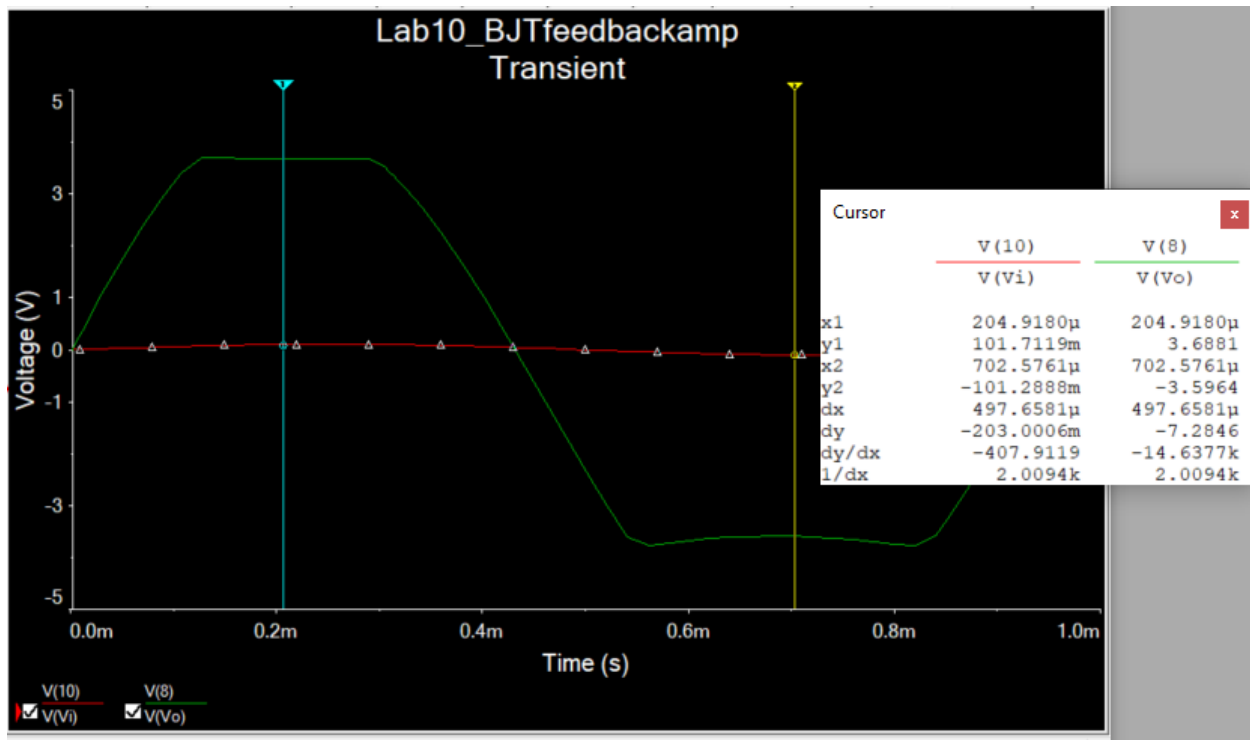


THD at above value

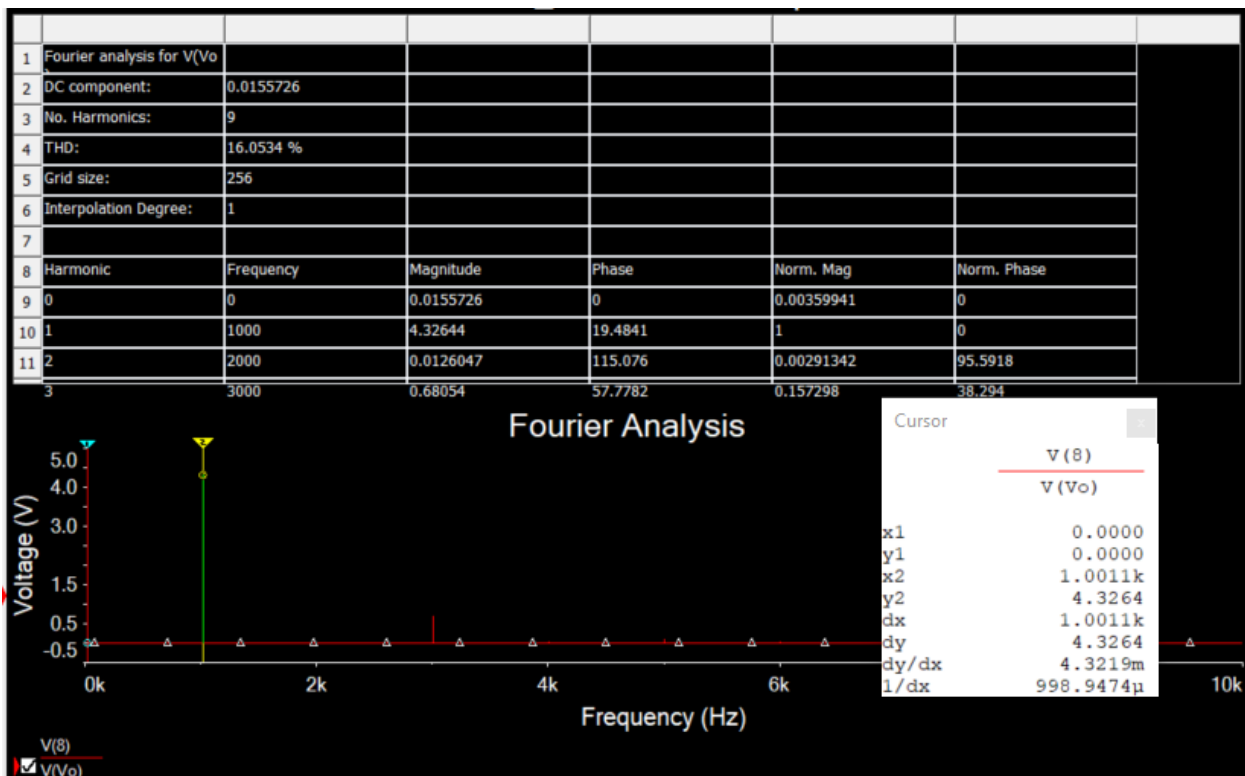


=16.05%

Measurements:


DcOp

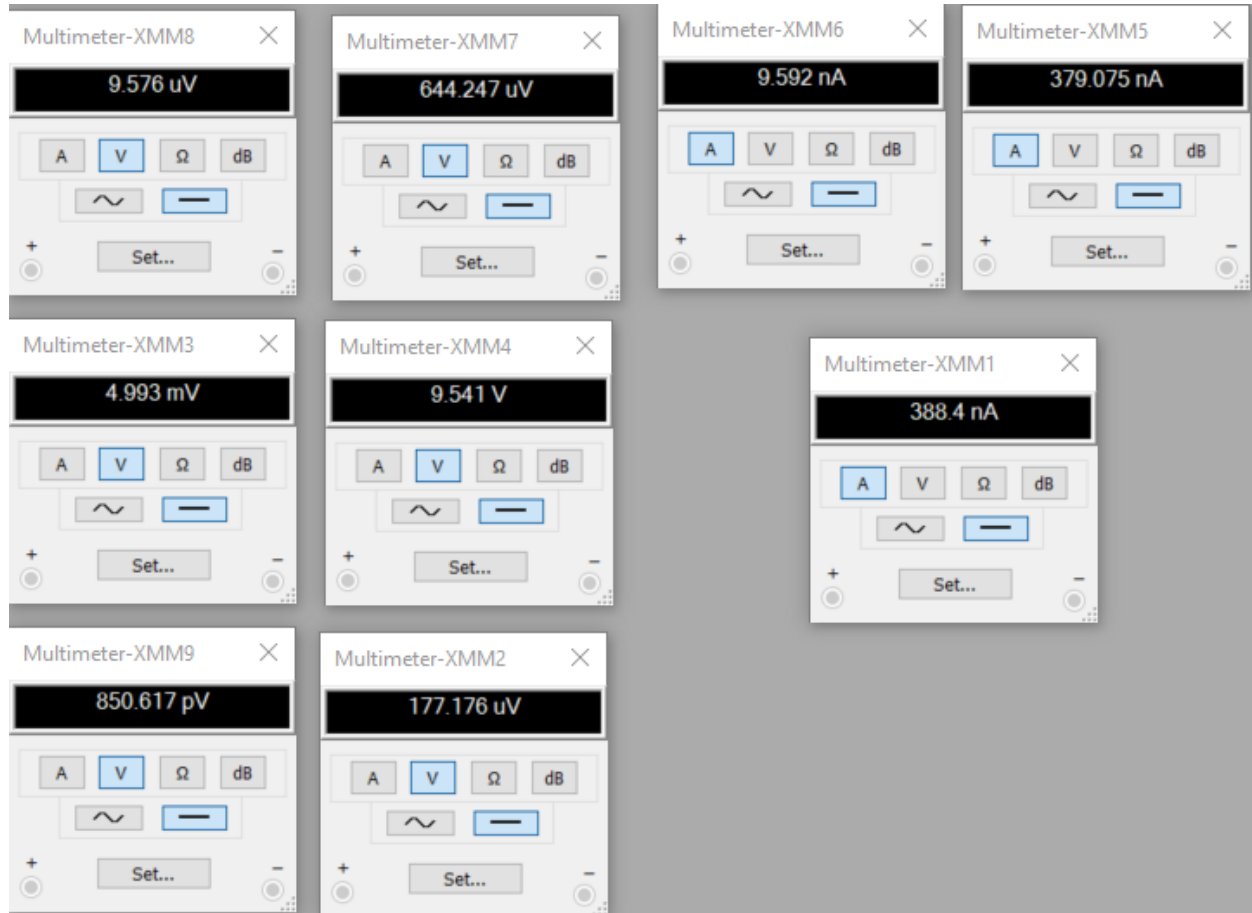

Gain

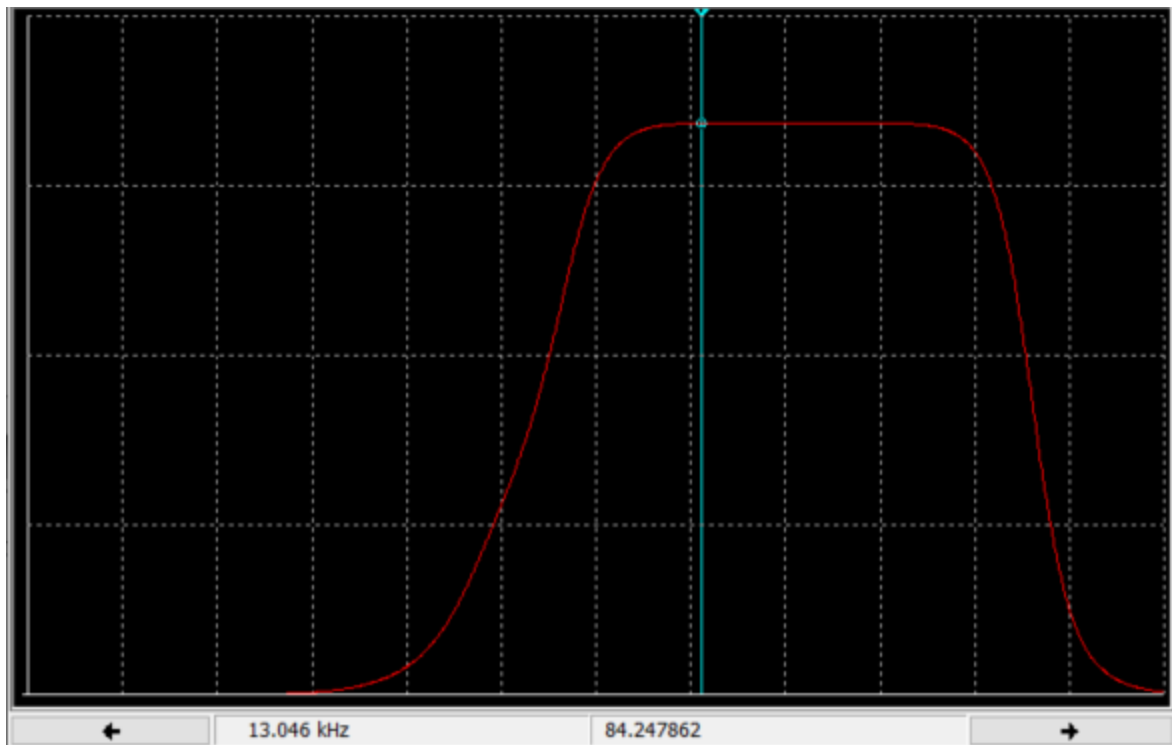


Rin

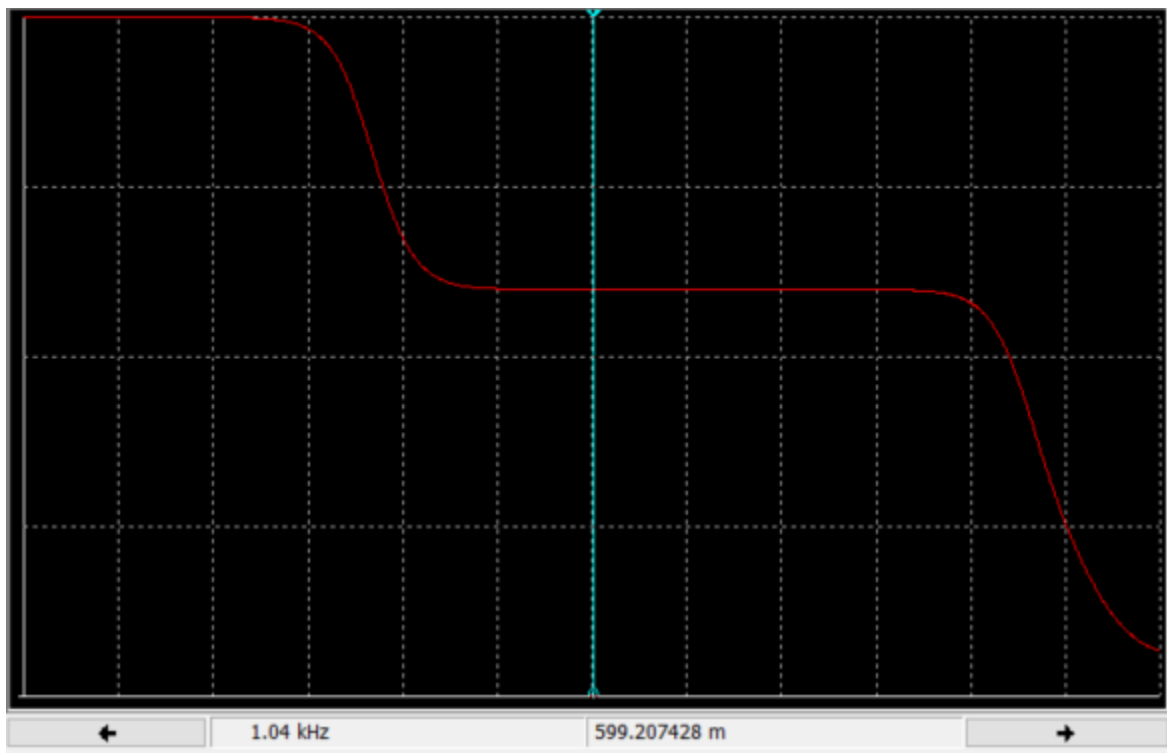


$=668\Omega$

Rout

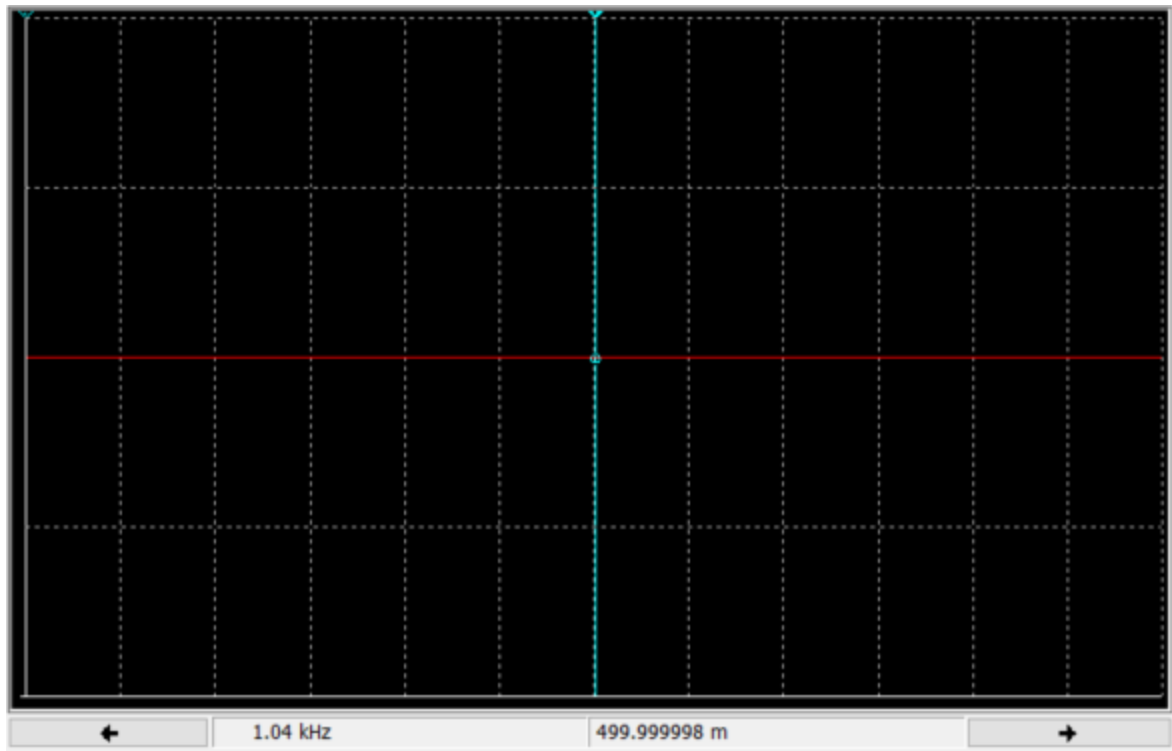


=10.04k Ω

Unclipped Output

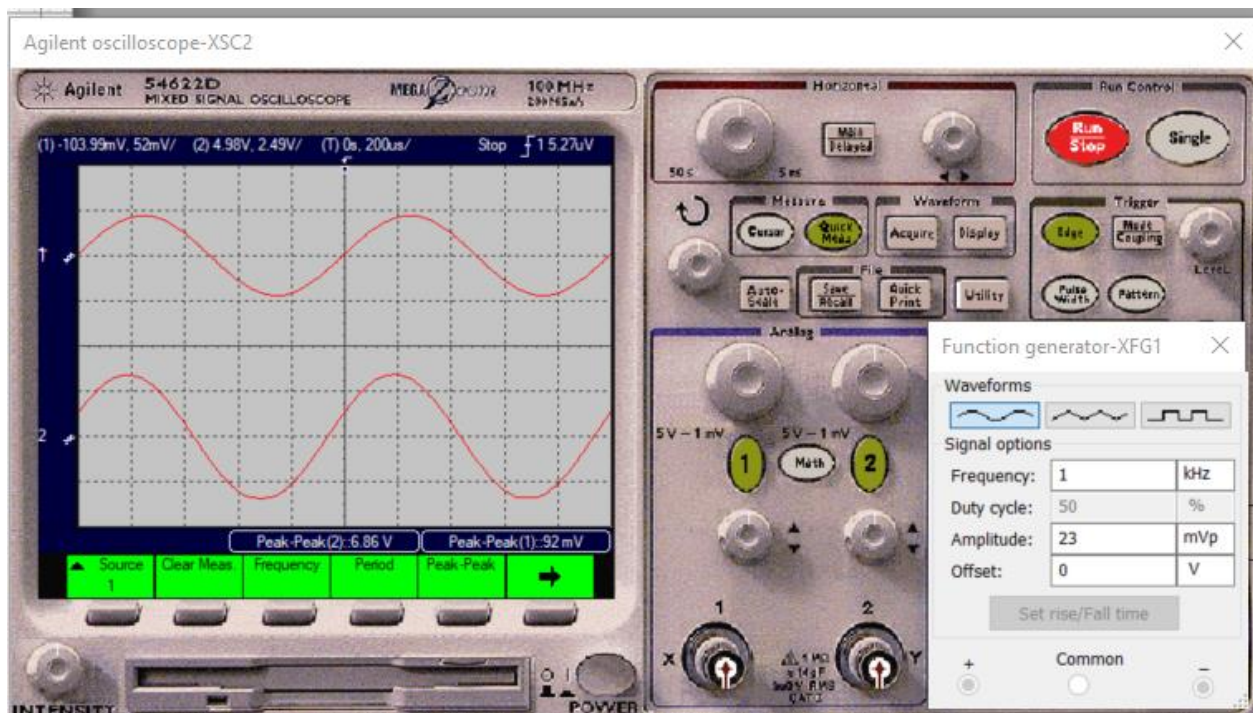

THD at that value

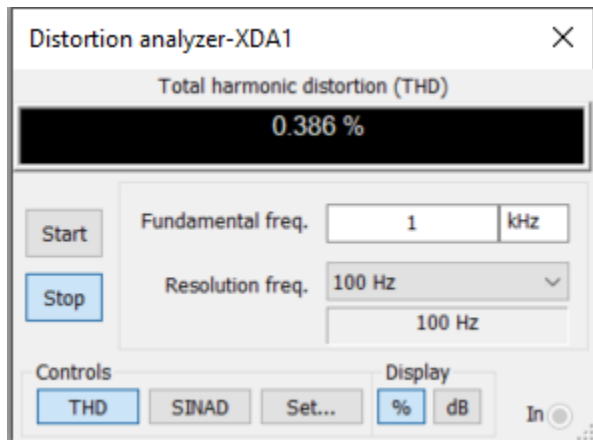

Results Discussed

	Calculated	Simulated	Measured
I _{supply}	<10mA	10.11mA	388nA
I _{c1}	7.6mA	7.575mA	9.502nA
I _{c2}	2.41mA	2.54mA	379nA
V _{c1}	-3.2v	-3.166v	9.578uv
V _{c2}	0.7v	0.681v	644.247uv
V _{b1}	-3.5v	-3.87v	4.9983mv
V _{b2}	-3.2v	-3.166v	9.3541v
V _{e1}	-4.5v	-4.599v	850.617pv
V _{e2}	-3.9v	-3.855v	171.176uv
Gain	~80	76	84
R _i	-	34Ω	668Ω
R _o	-	55Ω	10.04kΩ
Unclipped Swing	>3.5v	3.5v	3.5v
THD	-	16%	0.386%

The major differences come from the dc operation section of my work. This is more than likely just how the simulation will calculate the value with the measurements. I more than likely placed them improperly. The real work comes from the other aspects of the circuit. The input and output resistances are fairly different from each other however that is not a huge issue with the circuit.