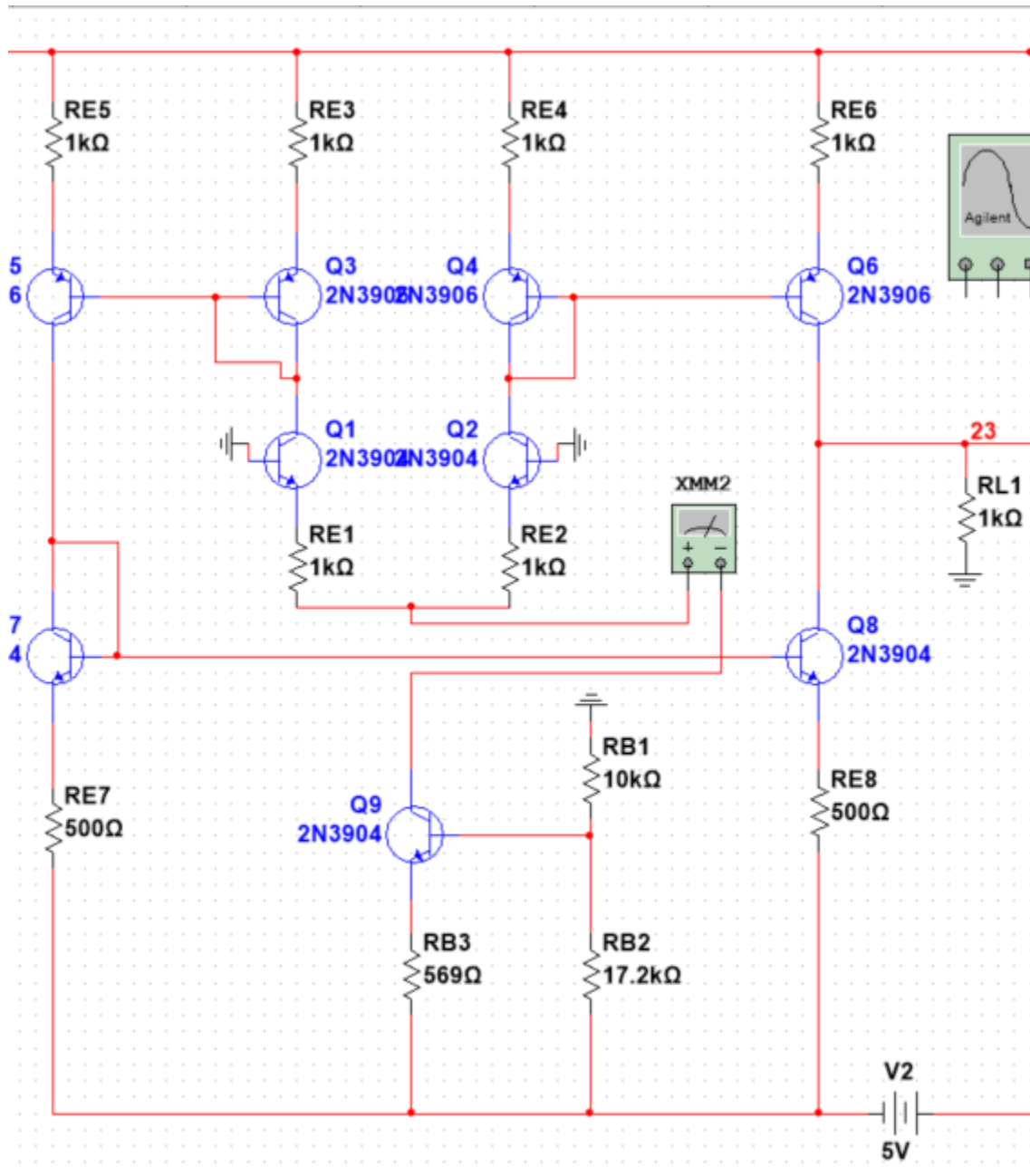


ECEN 326 – 501

## LAB 7: Operational Transconductance Amplifier

**Design:**




### Calculations:

DC Analysis

Lab #7

$Q_2 = Q_8$   
 $Q_5 = Q_6$   
 $Q_3 = Q_4$   
 $Q_1 = Q_2$

	NPN	PNP
Q <sub>5</sub> = Q <sub>6</sub>	2N3904	2N3906
Q <sub>3</sub> = Q <sub>4</sub>	140	180
Q <sub>1</sub> = Q <sub>2</sub>	75V	20V

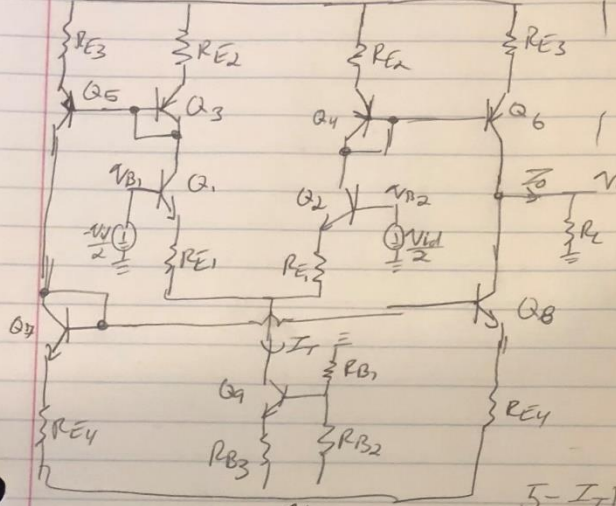

Requirements

$V_{CC} = V_{EE} = 5V$   
 $G_m = 1mA/V$   
 $V_{id,max} \geq 2V$   
 $V_{cm,max} - V_{cm,min} \geq 2V$   
 $f = 1kHz$   
 $I_{supply} \leq 5mA$

$I_T = 2mA$

$V_{id,max} = 2V = I_T R_{E1} \therefore R_{E1} = 2k\Omega$

$R_{B1} = 17.2k\Omega$   $R_{B2} = 10k\Omega$

$R_{B3} = 2.46k\Omega$

$\frac{I_{C5}}{I_{C3}} = \frac{R_{E2}}{R_{E3}}$

$5 - I_T R_{E2} - 0.2 > V_{cm} > -5 + I_T R_{B3} + 0.2 + I_T R_{E1} + 0.7$

$I_{C5} = 0.1mA$   $I_{C3} = 0.5mA$

$R_{E2} > 1k\Omega$   $R_{E3} = 5k\Omega$

$2.8V > V_{cm} > -0.96V$

$$r_{e2} = r_{e1} = \frac{V_T}{I_{E1}} = \frac{25}{0.5} = 50$$

$$r_{e4} = \frac{25}{0.5} = 50$$

$$r_{e6} = \frac{25}{0.5} = 50$$

AC

$$G_m = \frac{I_m}{V} = \frac{-I_{Sc}}{V_{id}} \rightarrow I_{Sc} = 1mA$$

$$I_{C4} = \frac{1V}{2k\Omega + 50} = 0.1187mA$$

$$I_{C6} = I_{C4} \cdot \frac{R_{E2} + r_{e4}}{R_{E1} + r_{e2}} = 0.101mA$$

$$I_{C5} = -0.101mA$$

$$I_{C8} = -0.10125$$

Second config

$$\frac{V_O}{V_S} = \frac{V_{cm}}{V_S + (V_{cm})} = 0.5$$

Third config


$$\frac{V_O}{V_S} = \frac{V_{cm}}{R_P + (V_{cm})} = 0.5$$

Simulations:


DcOp:

	Variable	Operating point value
1	-I(Q6:C)   I(Isc)	1.90433 m
2	I(V1:1)   I(Isupply)	-7.65591 m
3	I(Q9:C)   I(Itail)	3.86678 m

Gm:

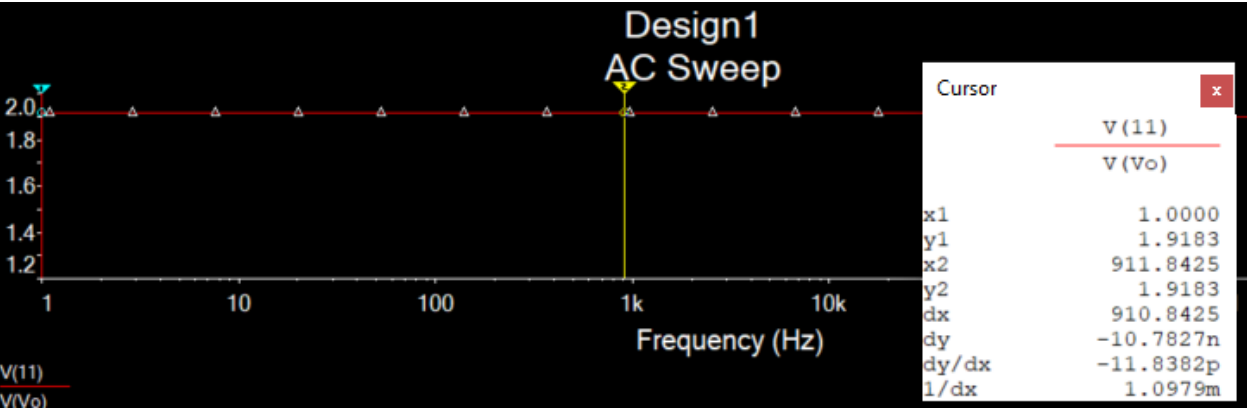


Rid:

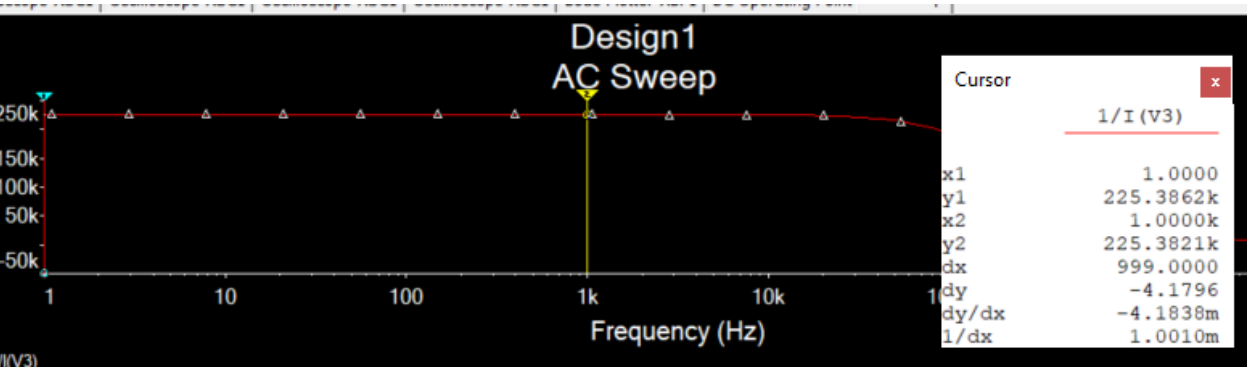


Measurements:

DcOp:

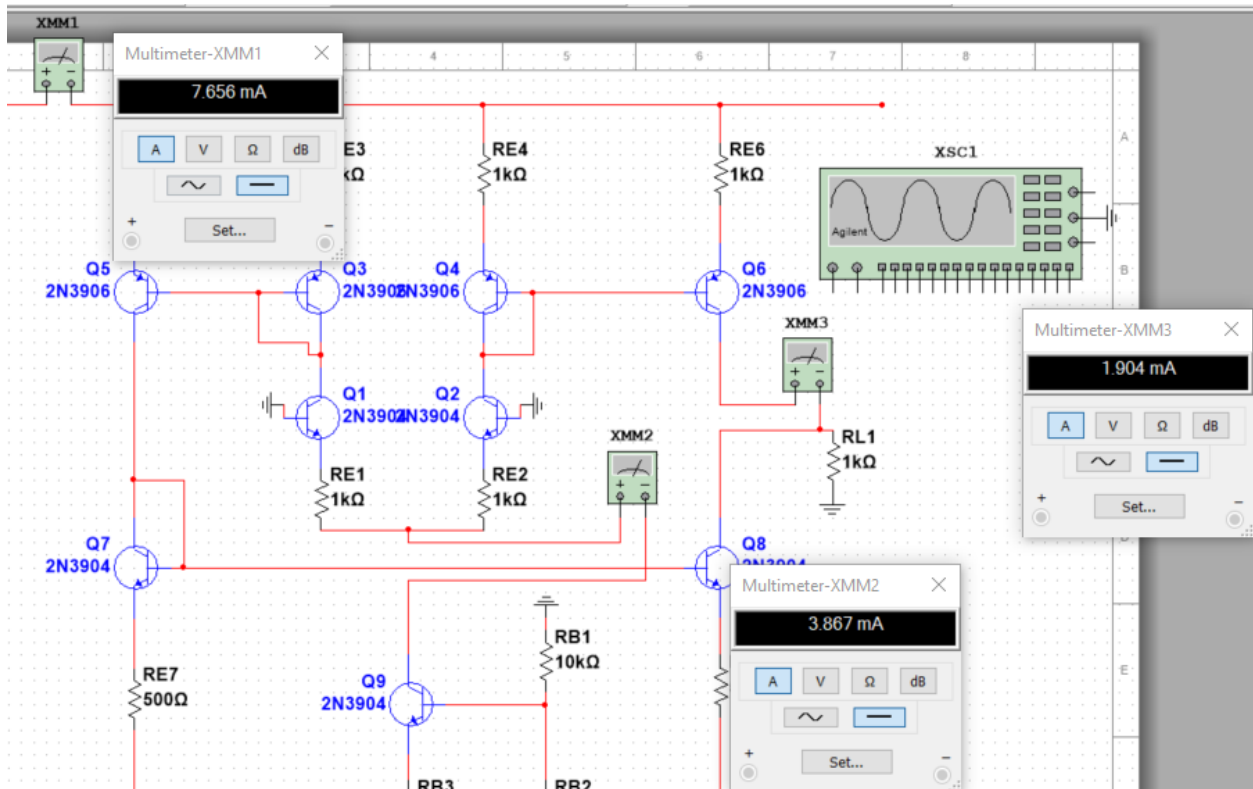


Gm

Oscilloscope-XSC1

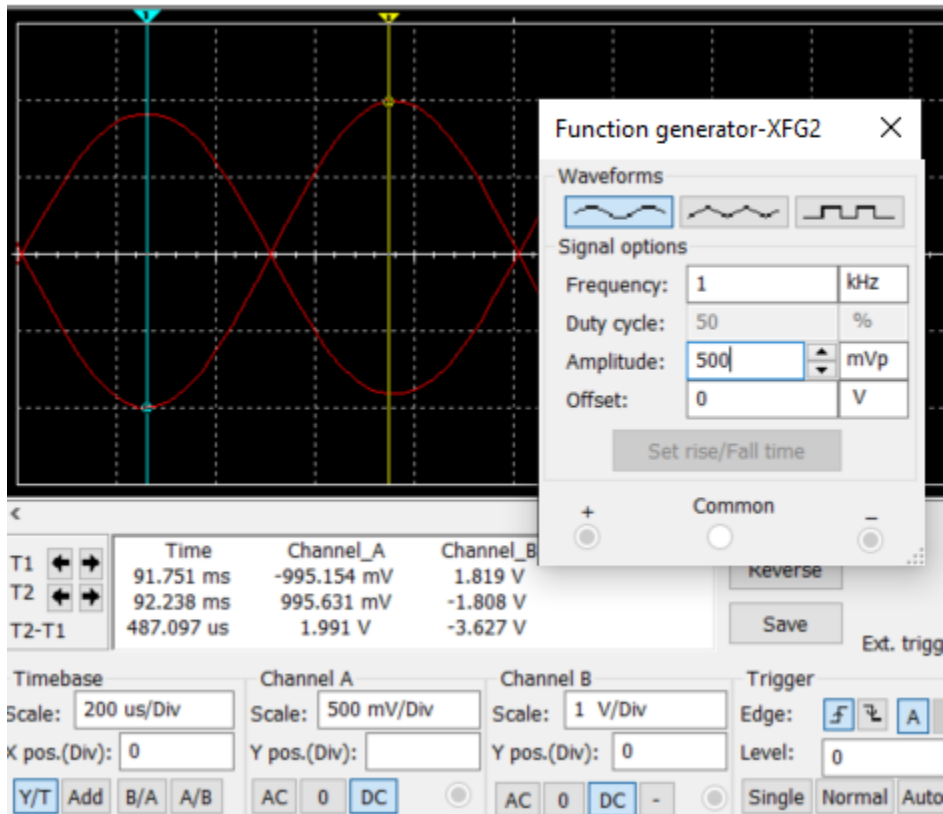


= 0.9113

Rid:

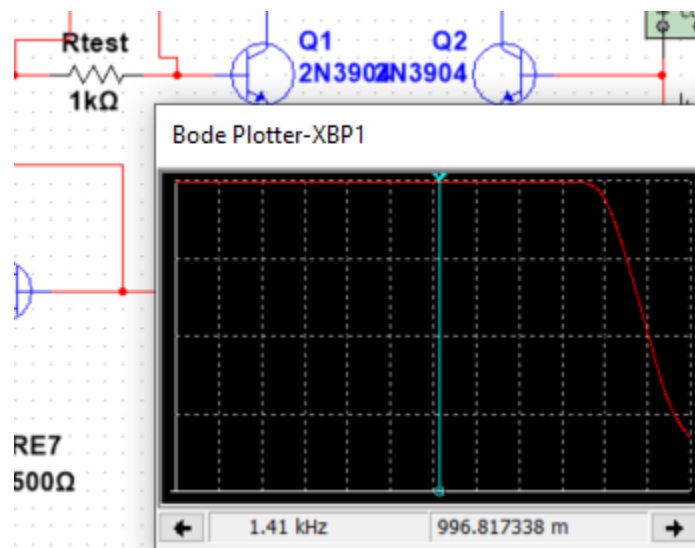


= 312.579kΩ


Vid max

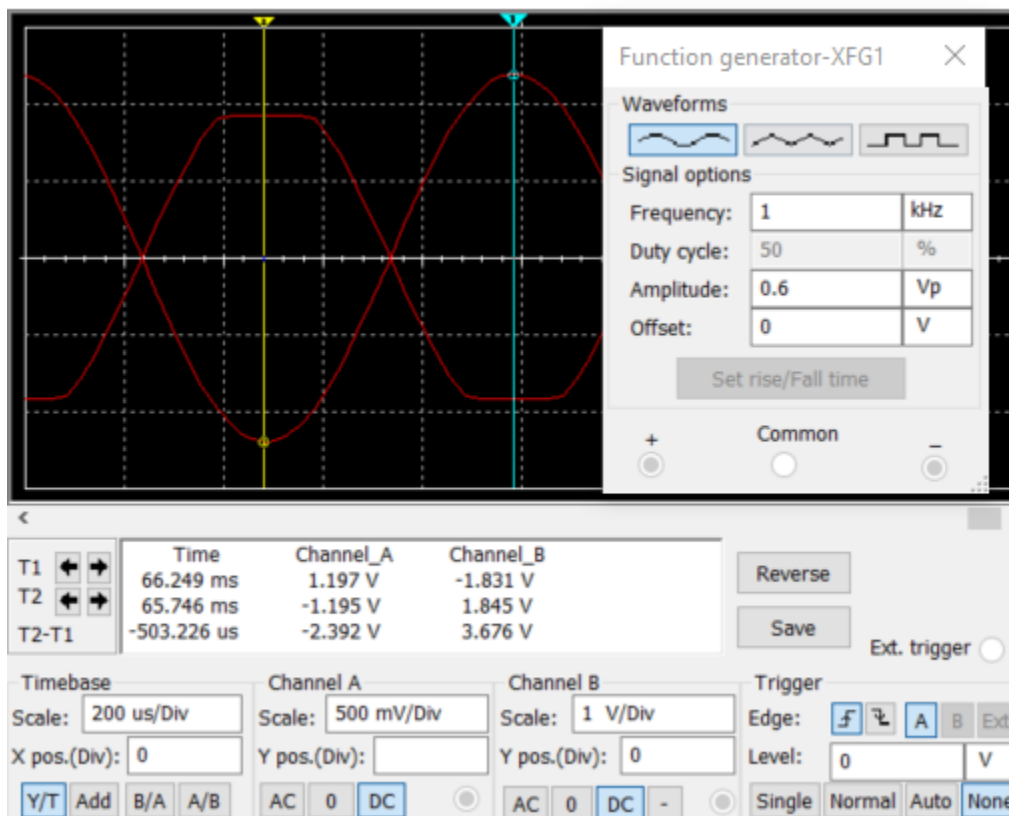

Gm Second Configuration:

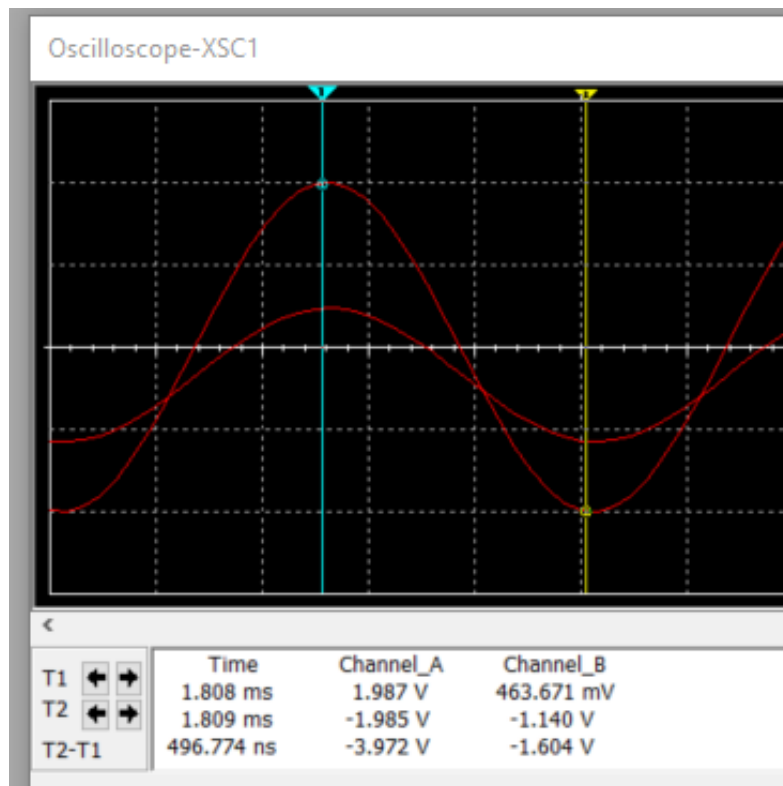


Gm Thrid Configuration:

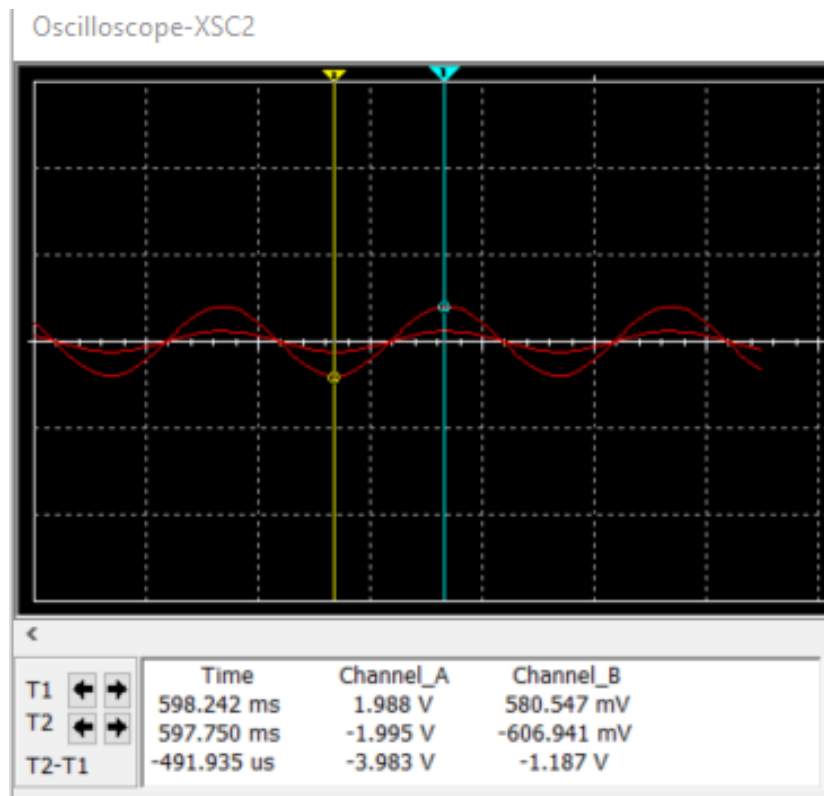


$V_{cm, max}$




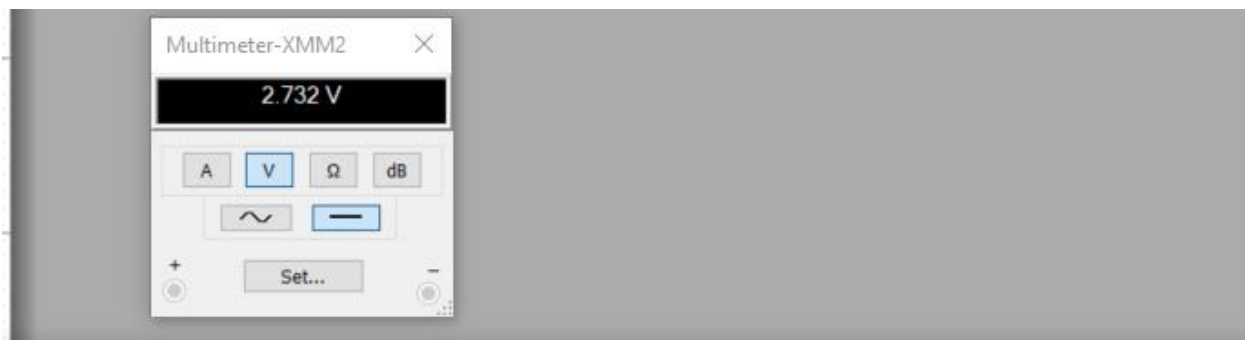

Agilent oscilloscope-XSC1

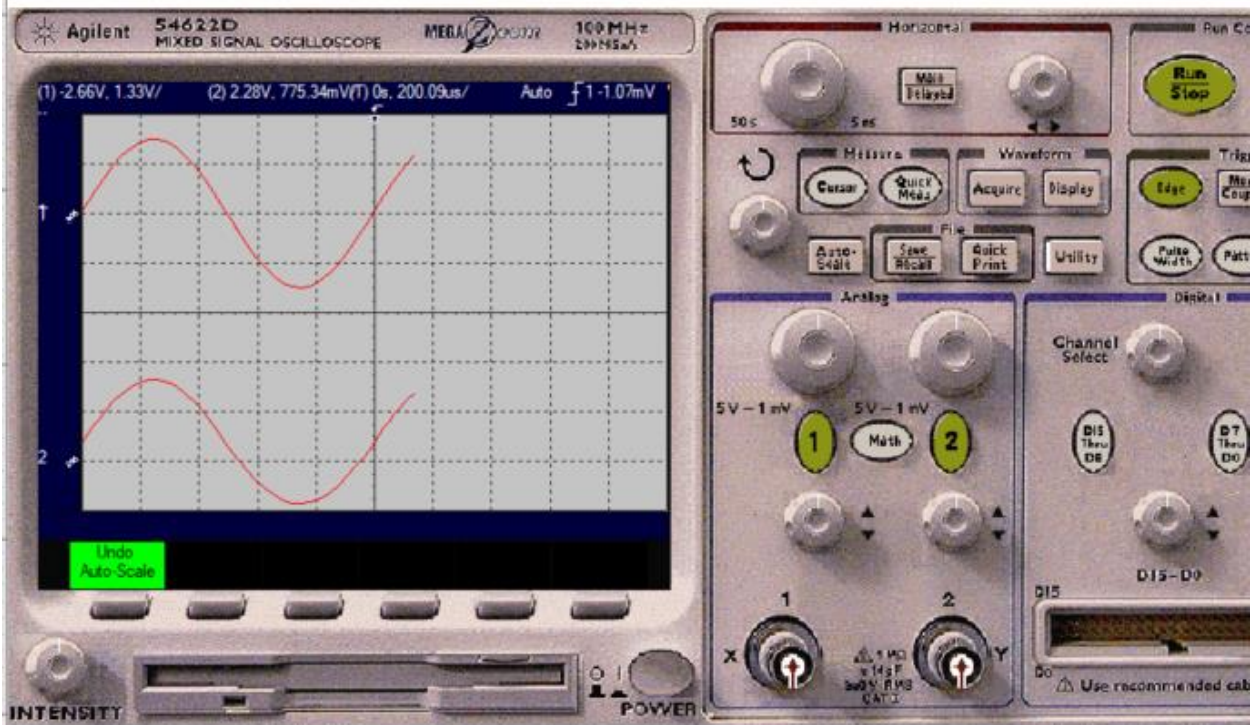

Vcm, min

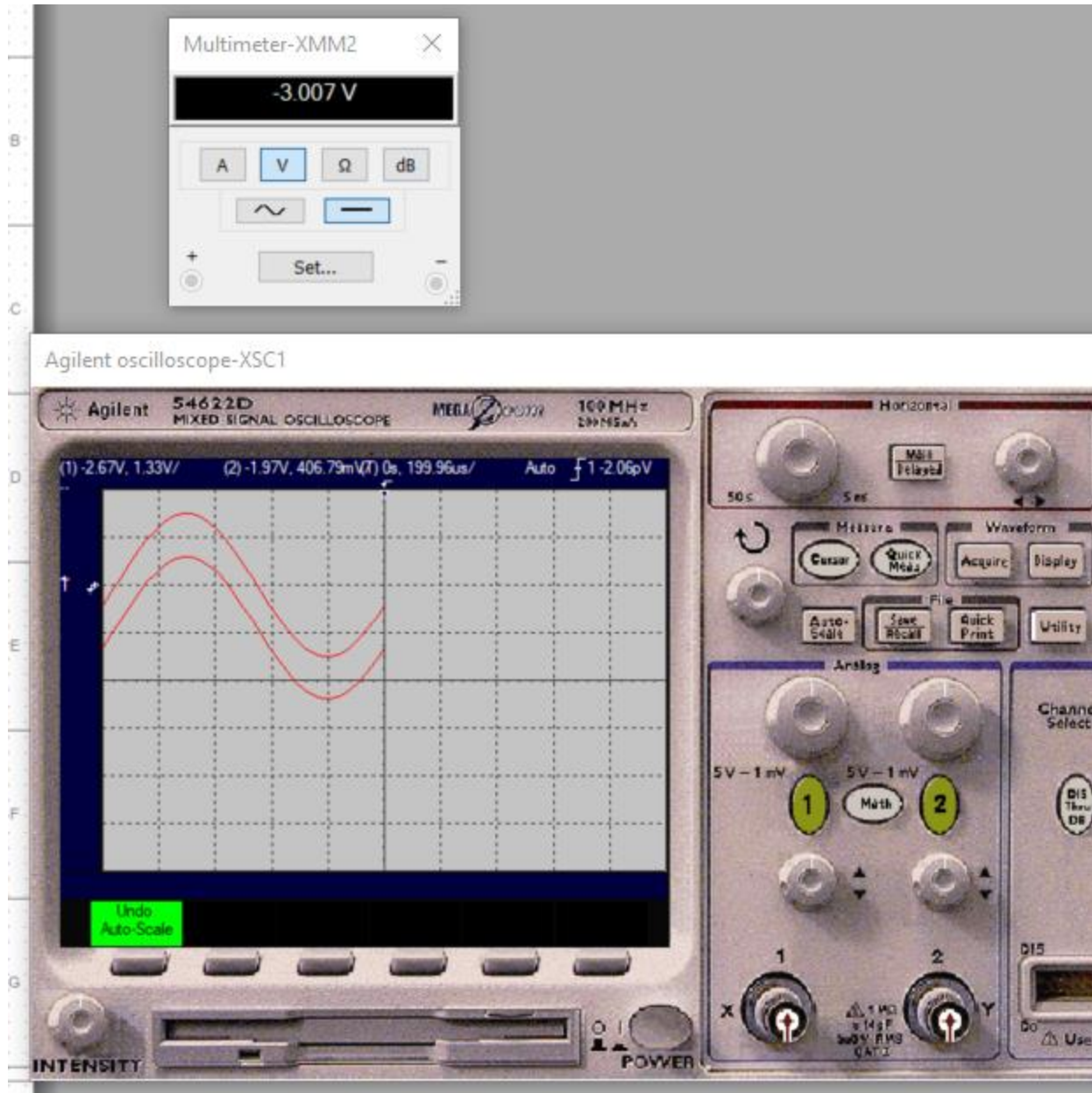

### Comparisons:

	Calculated	Simulated	Measured
Itail	2mA	3.84mA	3.867mA
Isupply	<5mA	7.6mA	7.658mA
Isc	1mA	1.9mA	1.904mA
Vid,max	>2v	-	0.6v
Rid	310.2kΩ	225kΩ	312kΩ
Vcm,min	-0.96v	-	-3.007v
Vcm,max	2.8v	-	2.73v



Gm,second	0.5	-	0.4038
Gm,third	0.5	-	0.298

Some key differences I found in my work were among the supply current measurements that I took. These values were slightly higher than allowed for in this lab so this more than likely created some errors in some of my other calculations. One of these calculations that I think it messed up was the common mode gain. The bounds for the upper limit were very similar to the calculated value however the lower limit was much lower than expected. This value still met the criteria for the lab however. The other area of concern was the current through the tail. This value was almost double what the calculated value was expected to be from the calculations. This is more than likely also tied to the problems with the supply current.