

Matthew Loden


ECEN 326-503

Lab 4: Design of a BJT Differential Amplifier


Procedure:

In this lab we designed a BJT differential amplifier with emitter resistors and a current source at the bottom.

Design:

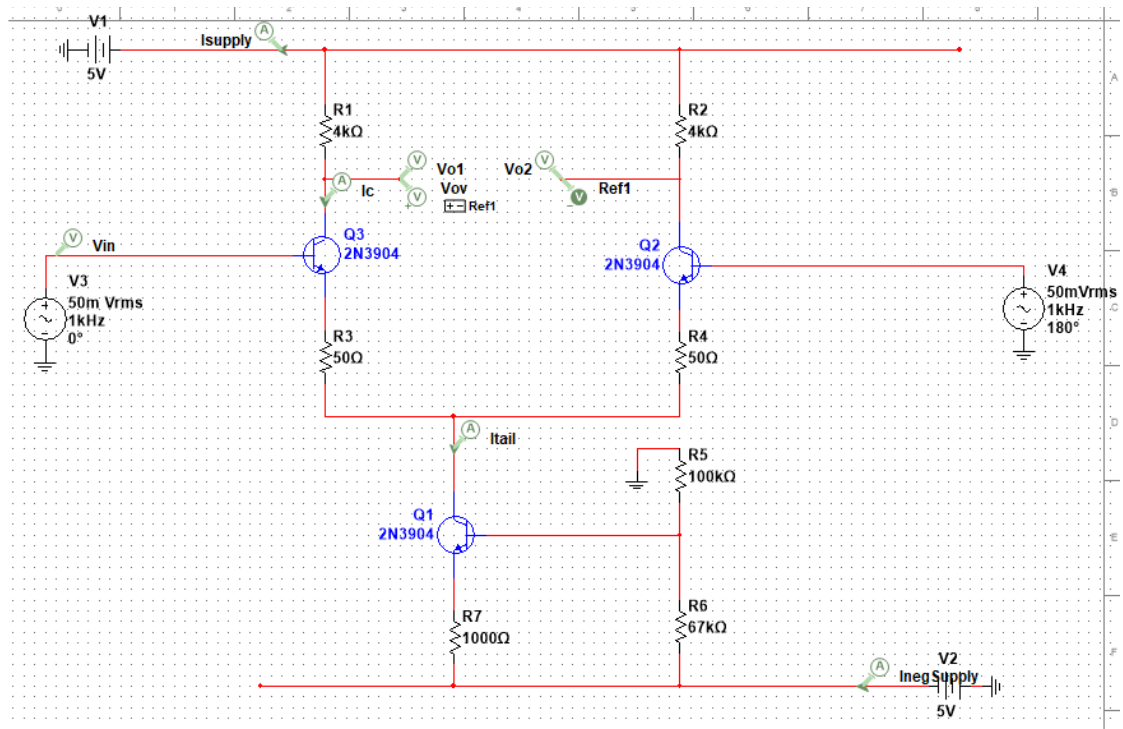

Calculations:

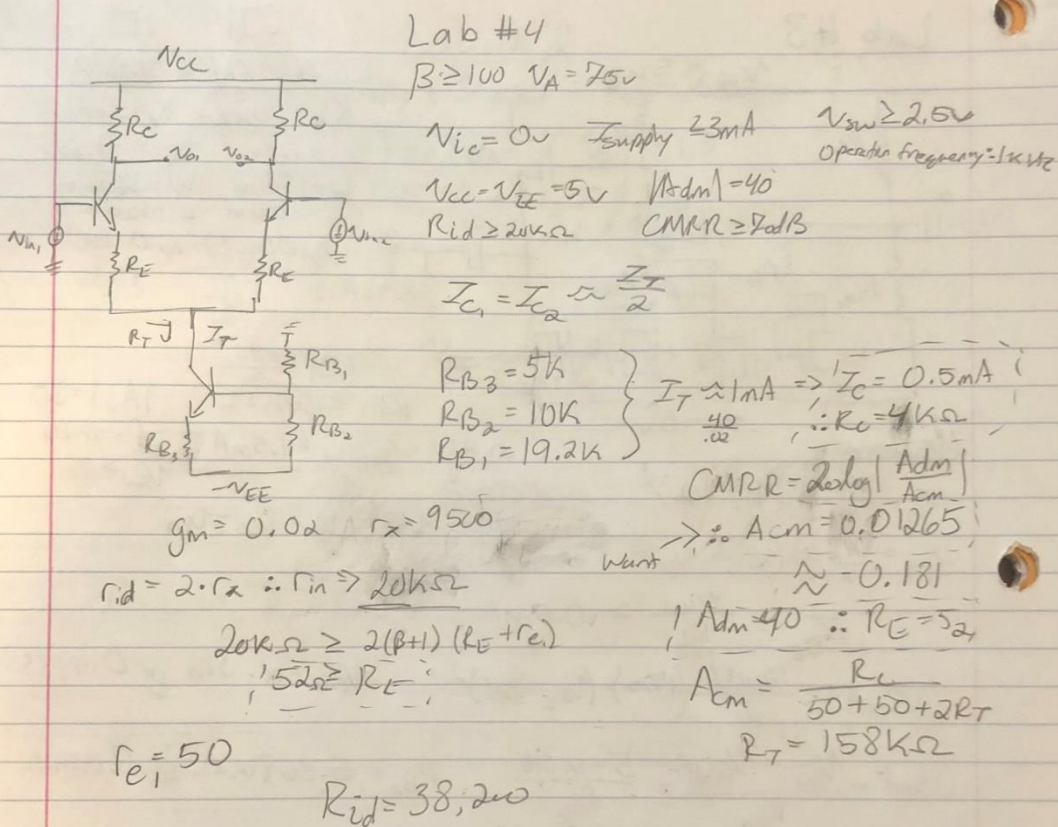


Simulations:


DcOp:

	Variable	Operating point value
1	I(Q3:C) I(Ic)	511.75850 u
2	-I(V2:2) I(InegSupply)	-1.06461 m
3	I(V1:1) I(Isupply)	-1.02352 m
4	I(Q1:C) I(Itail)	1.03166 m
5	V(10) V(Vin)	0.00000e+00
6	V(3) V(Vo1)	2.95297
7	V(9) V(Vo2)	2.95297
8	V(3) - V(9) V(Vov)	-7.10543e-15

Differential Gain:

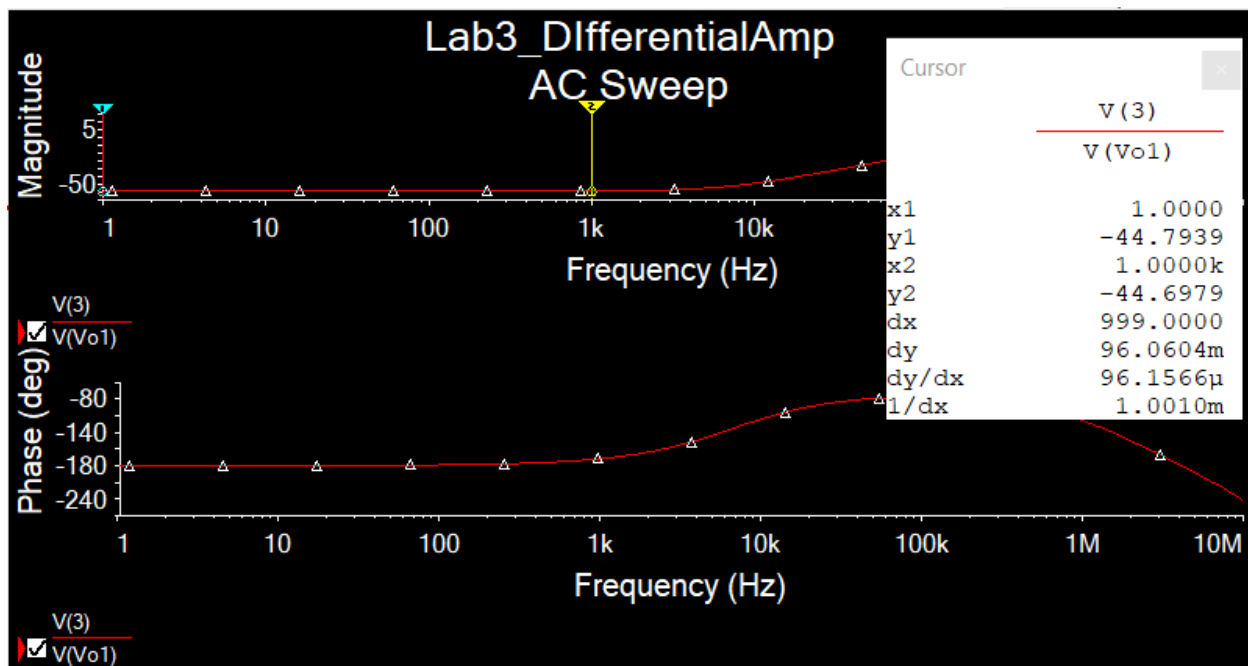


Rid:

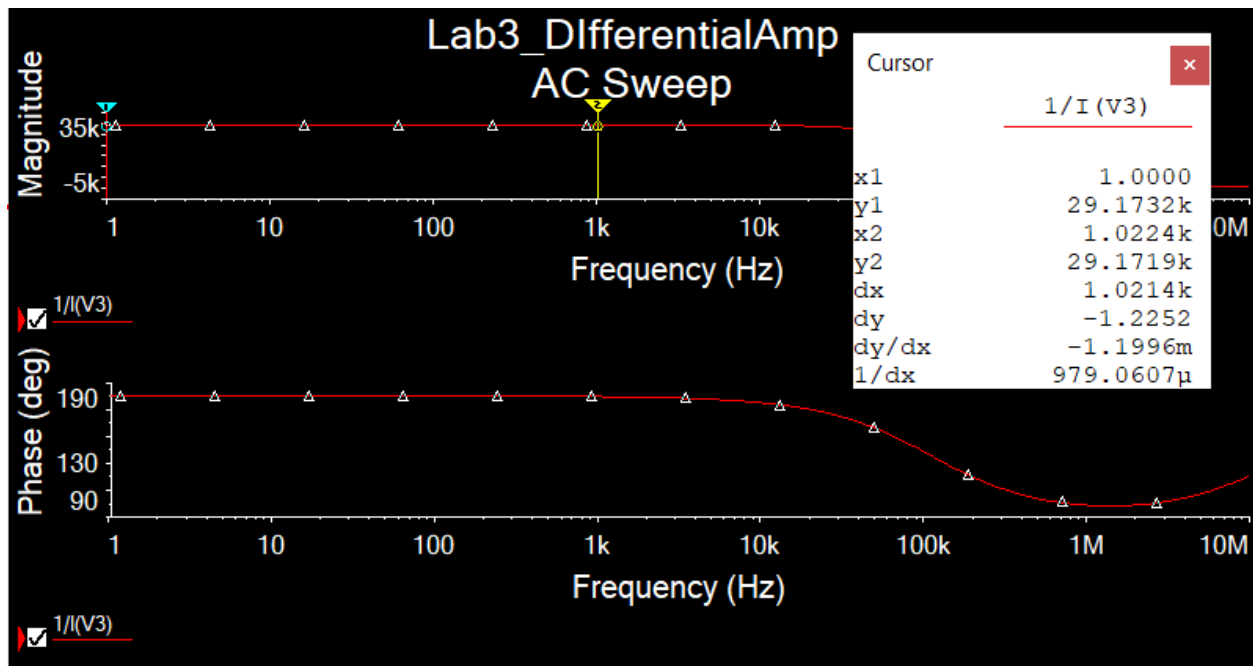


Measurements:


DcOp:

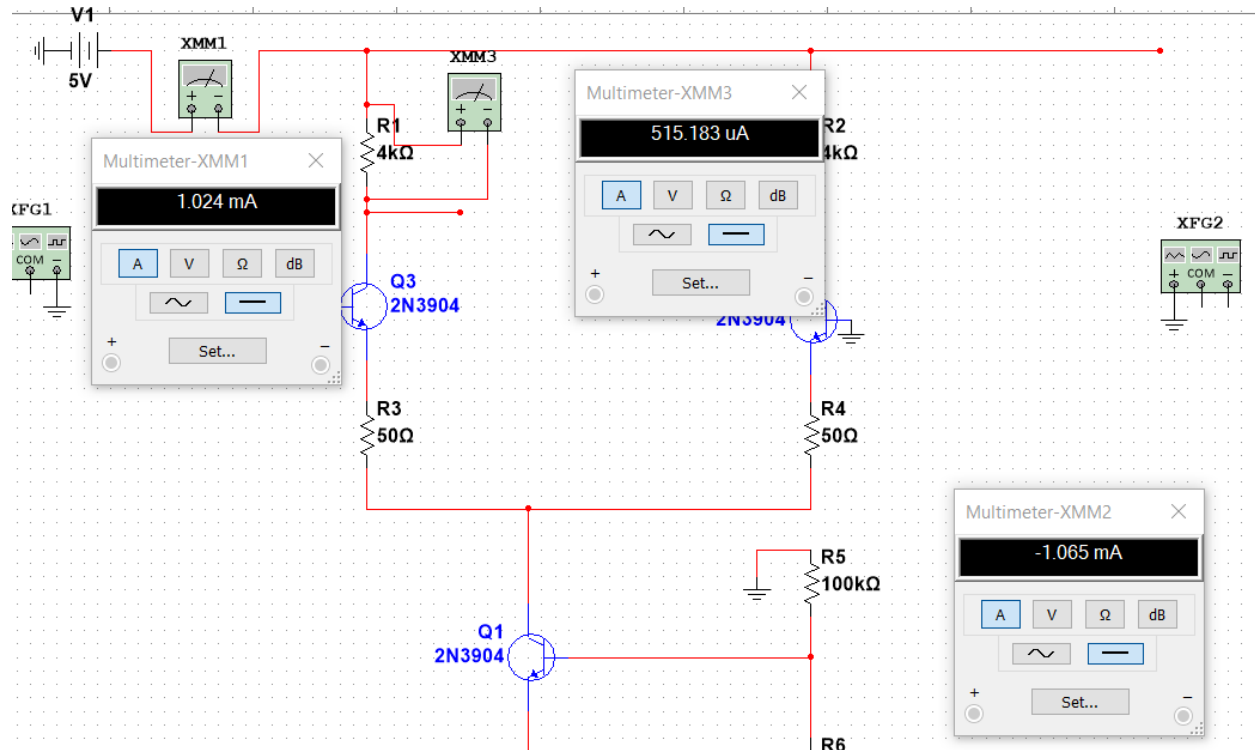


Vov:

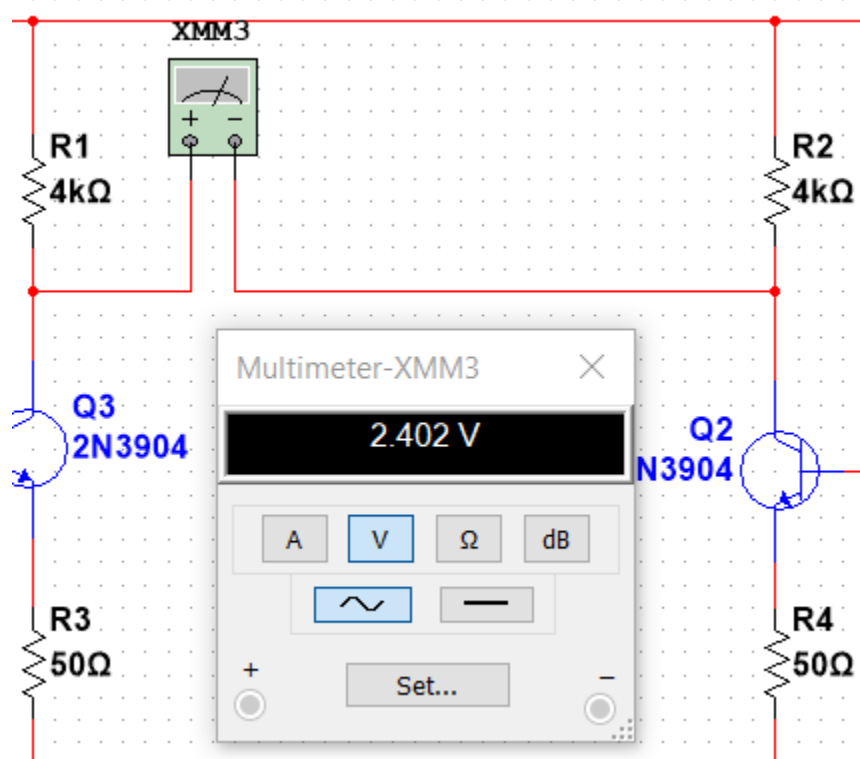


Unclipped Swing

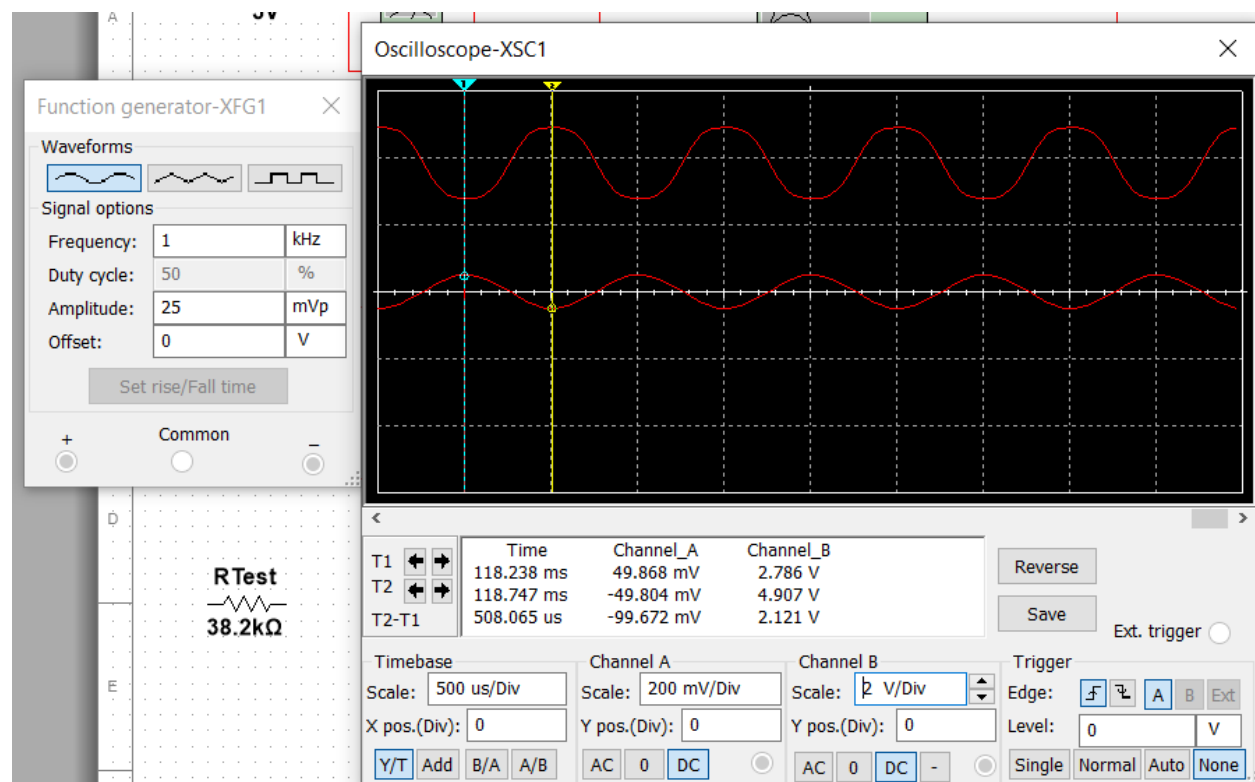

Adm:

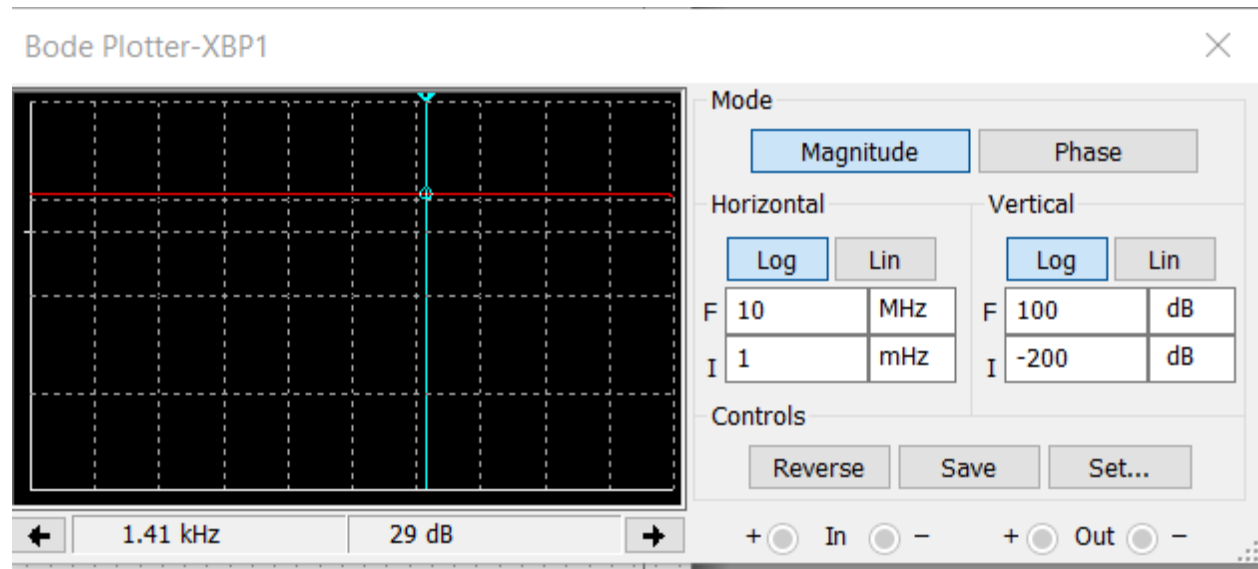


Rid ratio @ Rtest = 38.2k:

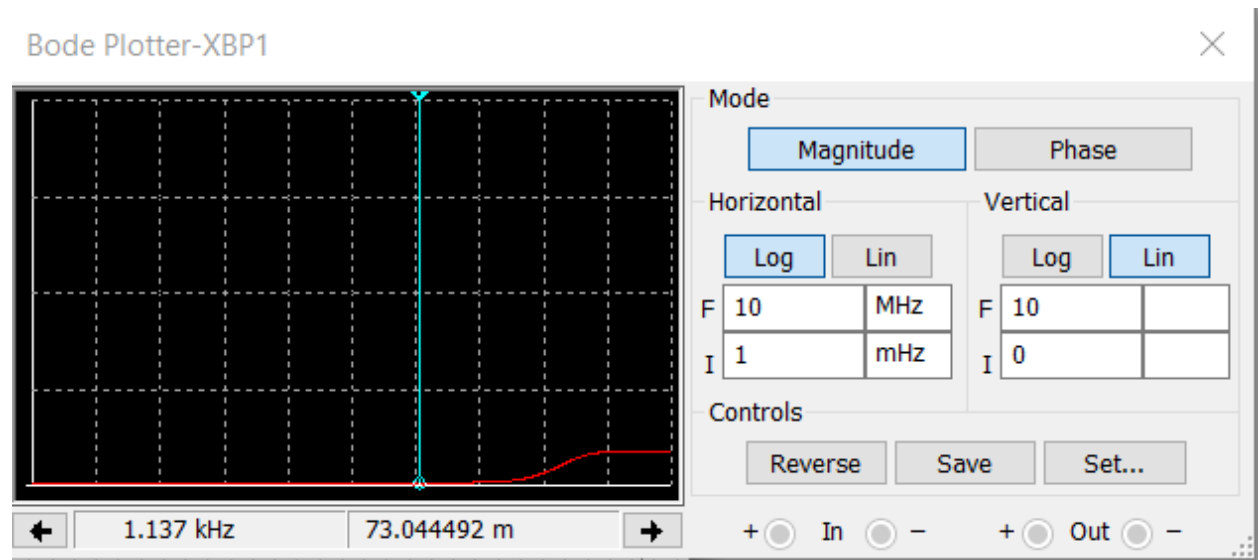


Rid = $3k * 2 = 6k$

THD @ 1%:

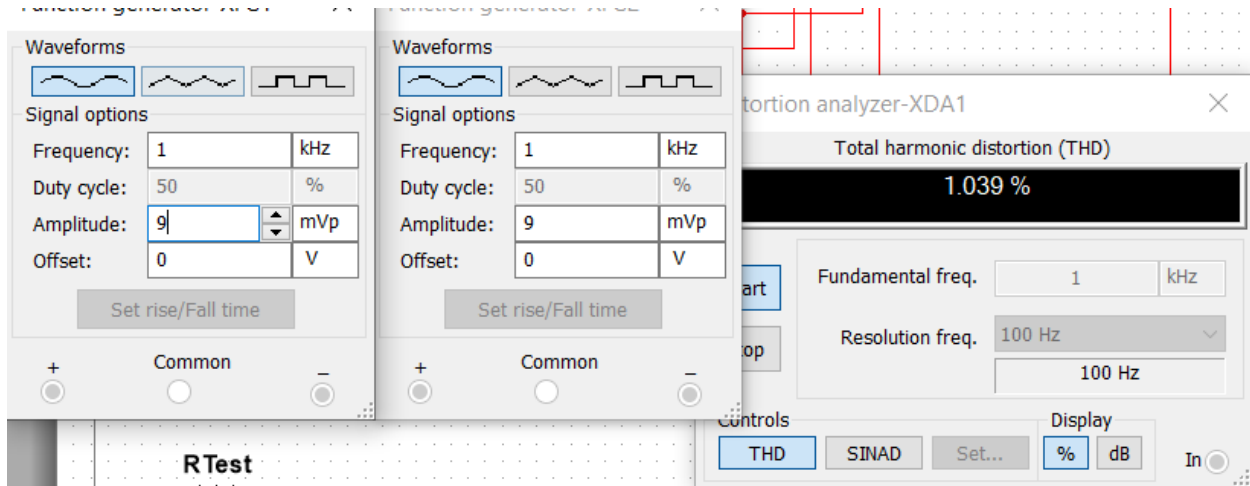

THD @5%:

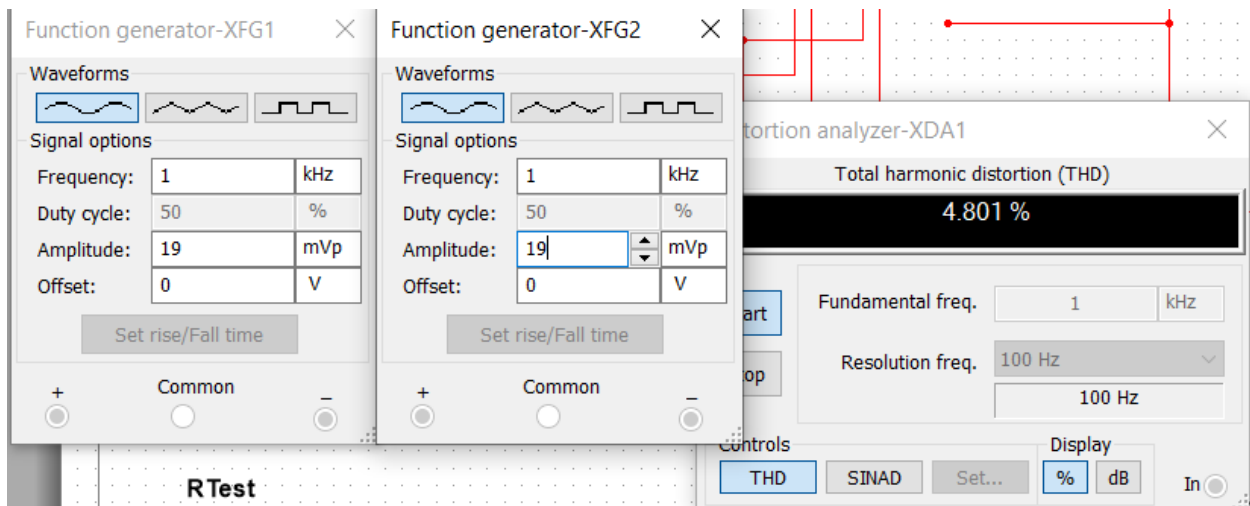

Common Mode Gain:

Results:

	Calculated	Simulated	Measured
Itail	1mA	1.03mA	$2 \cdot I_c = 1.03\text{mA}$
Ic	500uA	511uA	515uA
Isupply	1mA	1.03mA	1.024mA
Vov	0v	0v	2.4v
Adm	40dB	44.69dB	29dB
Acm	0.01265	-	-
Rid	38.2k Ω	29.17k Ω	6k Ω
Unclipped Swing	2.5v	2.03v	2.12v

A big difference in my data comes from the differences between my measured data and my simulated/calculated data. My simulations line up very similarly to what I've calculated however when I switch my instruments over to the measurements the numbers start to go a little crazy. For starters, the voltage difference from the output 2 – output 1 is zero when the circuit is in differential mode however when measured it outputs around 2.4 volts for some reason. I'm not sure if this has something to do with how the simulation deals with grounded sources or if there was something that was miscalculated. Another smaller difference comes from the gain, where the simulated is above the calculated value and the measured is noticeably below. There is about a ten dB drop from the simulated differential gain to the measured gain which is significant however I'm not sure what has caused this. I again think this might have something to do with the way the simulation deals with ACsweep vs the bode plotter. The input resistance is my largest difference with a reasonable calculation value, a higher than minimum simulated value and an incredibly low measured value. The measured value is so low that it isn't even meeting the minimum requirement for this amplifier. Finally, my common mode gain was something that I could not figure out how to calculate for this lab. I tried running the simulation with the two inputs voltages connected and producing the same signal however I only could measure large values with that. I know that this value must be very small so that the CMRR can be large, and I know that the value should be very small when the circuit is mirrored correctly so I think my value should be right however I don't know how to measure it.